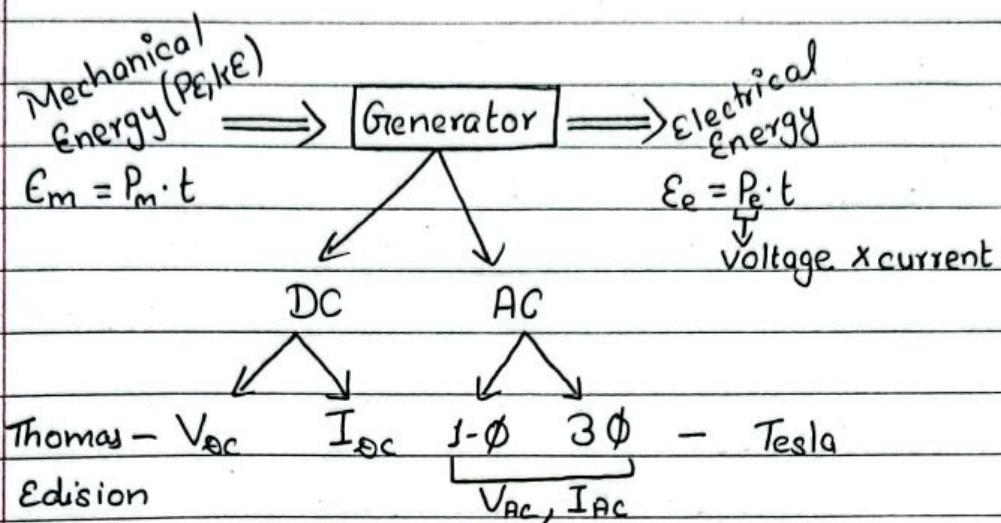


Chapter 1:

Fundamental of Electrical Energy.



* CURRENT

The rate of change of charge is known as current.


$$i = \frac{dq}{dt}, \quad dq \rightarrow \text{charge}, \quad dt \rightarrow \text{time}$$

$$\dot{q} = n \cdot e$$

unit = Ampere = C/sec

* VOLTAGE / POTENTIAL DIFFERENCE

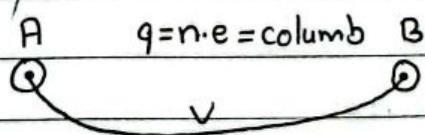✓ Voltage is a measurement between two points of any electrical element i.e. it can be also defined as the pressure due to which electron moves from one point to another point.)




$$\text{Electrical pressure } = v = \frac{dw}{dq} = \frac{1 \text{ Joule}}{1 \text{ coulomb}} = 1 \text{ volt.}$$

* | POWER

The power 'p' is nothing but the time rate of flow of electrical energy which can be written as

$$P = \frac{d\omega}{dt} = \frac{d\omega}{dq} \times \frac{dq}{dt}$$

$$P = V \cdot I$$

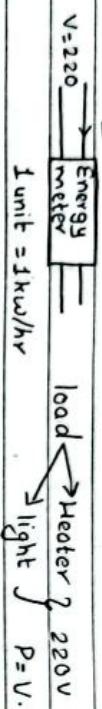

Example : heater $\Rightarrow P = 1\text{kW}$


$$\text{Energy} = P \cdot t = 1\text{kW} \times 1\text{hr}$$

$$= 1\text{kWhr}$$

$$= 1\text{unit.}$$

* Circuit Variables

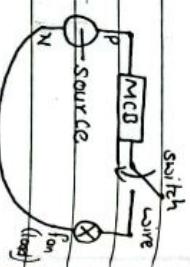
- 1) Source (Battery, cell, generator)
- 2) Load (TV, Heater, Freezer, washing machine)
- 3) Wire (Copper, Aluminium)
- 4) Safety device (fuse, MCB, MCCB)
- 5) Controlling unit (switch, regulator).



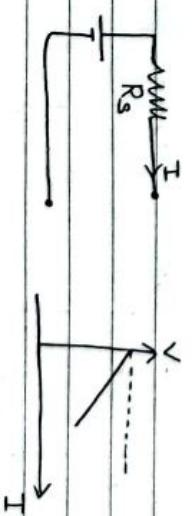b) Practical Voltage Sources.

All practical voltage source fall short of an ideal source and terminal voltage falls with increase in the current supplied by the sources.

Hence a practical source is represented by voltage source in series with internal resistance 'Rs'.



(Graphical representation)



i) Voltage source

ideal voltage source

Ideal voltage source is a source which delivers energy with specified terminal voltage, which is independent of the current supplied by the source.

Electrical sources : which supply electrical energy.

A. Independent source

- i) Voltage source
- ii) Current source.

Passive element can't deliver power to other elements,


however they can absorb power.

e.g : resistor, inductor, capacitors

b) Heat form
b) magnetic
field

b) electric field.



terminals.

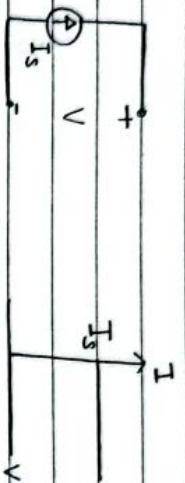

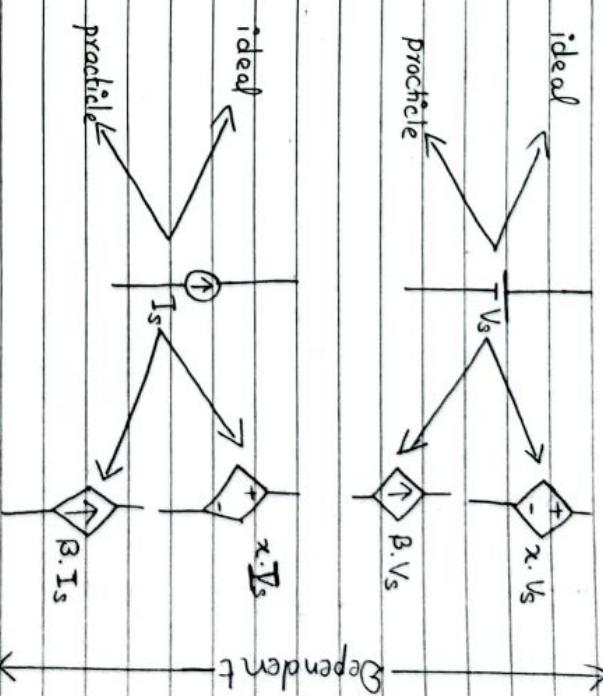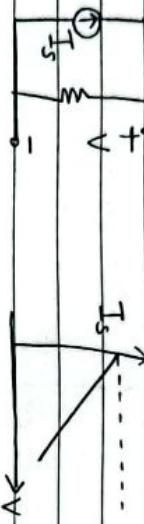b. Practical Current Source


This is represented by the current source I_s in parallel with internal resistance.

In this, current is supplied by the source is decreased with increased in voltage.




* Source Transformation

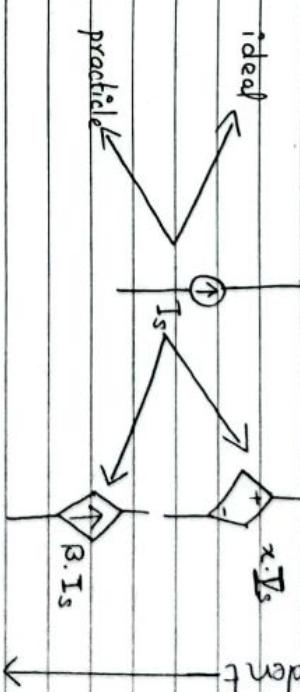1. Voltage source converted to current source.



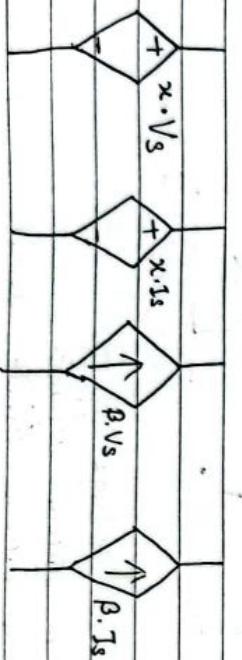B. Dependent Sources
A dependent source can be represented by diamond shape symbol.
There are four types, which are :



Voltage source.


current source.

$$\text{e.g. } \begin{matrix} 10V \\ \text{---} \\ 2\Omega \end{matrix} \Rightarrow \begin{matrix} \oplus \\ I_s \\ \text{---} \\ R_s = 2\Omega \\ I_s = \frac{V_s}{R_s} = 5A \end{matrix}$$

2) Current source converted into Voltage source.

$$R_s$$

$$\text{A}$$

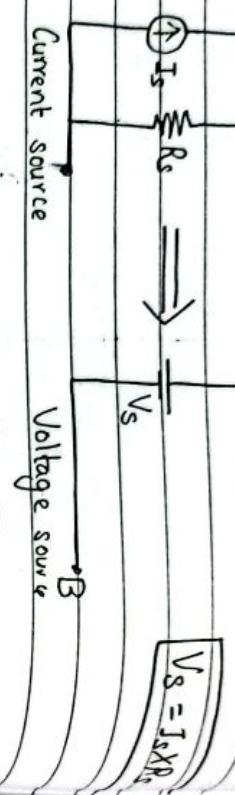

Current source

Voltage source

$$\text{e.g. } I_s = 10\text{A} \quad R_s = 2\Omega \quad \Rightarrow \quad V_s = I_s \times R_s$$


$$= 10 \times 2$$

$$= 20\text{V}$$

20-January.

* DC Circuits

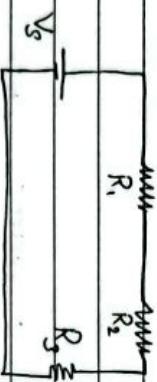An electrical circuit is a closed path consisting of active and passive elements all interconnected and current flows in a closed path.



$$V = IR$$


$$V = I_s \times R_s$$

$$= 10 \times 2$$

$$= 20\text{V}$$

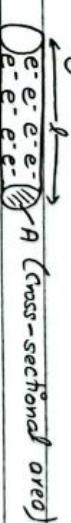i) Resistor

It is an electric element which opposes the flow of electrons through it.



$$R \propto \frac{1}{A}$$

$$R \propto \frac{1}{A}$$

$$\therefore R = \rho \frac{l}{A} \quad [(\rho) = \text{resistivity [electrical properties]}]$$

unit of Resistance : (Ω) ohm.

Resistance also depends on heat / temperature.



Active element supplies energy to the circuit.
Passive element receives energy from the circuit.

This energy is converted to heat (resistor) or stores it in energy electric (capacitor) or magnetic field (inductor). Battery is the active element.

Basic Circuit Components

There are three basic components which are as follows:

i) Resistor if it absorbs energy in heat form.

ii) Capacitor if energy store in magnetic form

iii) Inductor if energy store in electric field form.

Symbol :

$$\frac{di}{dt} = \frac{V}{R}$$

- i) Capacitor
Capacitor is a storage element which can store and deliver energy in an electric field.

$E_{\text{dielectric}} = \frac{C}{d} \cdot V$

$C = \epsilon \cdot A / d$

unit of capacitance → farad (F)

Symbol



Non-polar capacitor



Polar capacitor

iii) Inductor

Inductor is a storage element which can store and deliver energy in a magnetic field.

$L = N \cdot \phi / I$

N - number of turns
 ϕ - magnetic flux
 I - current

Unit of Inductor : Henry ('H')

Symbol:

$$L = N \cdot \phi / I$$

XX Ohm's law:

When a voltage is applied to a closed path or circuit it causes a flow of electrons and there exists, current in the circuit. The resistance of the circuit opposes the current flow.


Statement : When the temperature remains constant, current flowing through a conductor is directly proportional to the potential difference across the conductor.

i.e. $V \propto I$ (at least constant temperature)

$V = I \cdot R$; where R = proportionality constant


V = Voltage in Volt.

I = current in Ampere.

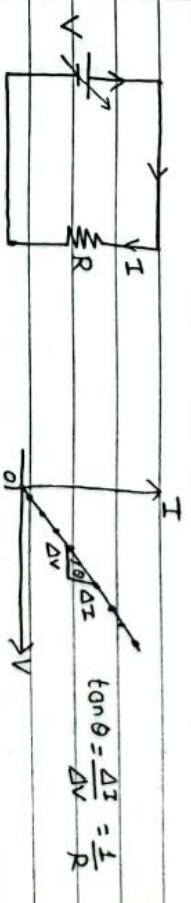

Limitations :

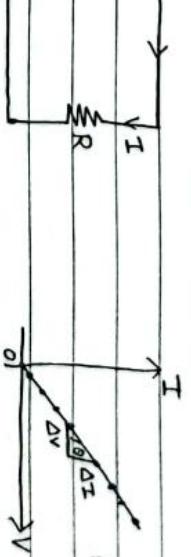1. It is not applicable to non-metallic conductors.
2. It is not applicable to non-linear devices like zener diodes, vacuum tubes etc.
3. It is not applicable if the temperature changes.




Classification of electrical circuits :


→ Series




→ Parallel

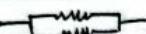

→ Series parallel

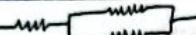


→ Mesh Network.

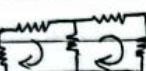

// Resistor

a) Series

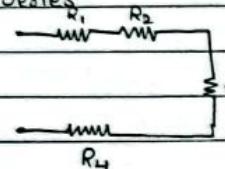


$$R_{eq} = R_1 + R_2 + R_3 + R_4 \dots \dots$$

→ current same ($I_1 = I_2 = I_3 = I_4 \dots$)

→ Voltage different (V_1, V_2, V_3, V_4)

b) Parallel

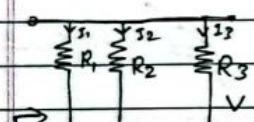


→ current different (I_1, I_2, I_3)

→ Voltage same ($V_1 = V_2 = V_3 = V$)

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

// Capacitor

a) Series

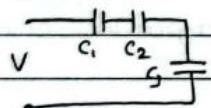

$$V = V_1 + V_2 + V_3$$


$$Q = C \cdot V \\ = \frac{Q_1}{C_1} + \frac{Q_2}{C_2} + \frac{Q_3}{C_3} \\ V = Q/C$$

$$Q_1 = Q_2 = Q_3 = Q_4$$

$$V = Q \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)$$

$$\frac{V}{Q} = \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

b) Parallel

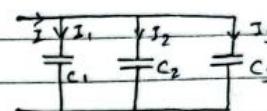

$$I = I_1 + I_2 + I_3, V = V_1 = V_2 = V_3$$

$$Q = Q_1 + Q_2 + Q_3$$

$$= C_1 V + C_2 V + C_3 V$$

$$Q = (C_1 + C_2 + C_3) V$$

$$\frac{Q}{V} = C_1 + C_2 + C_3$$


$$C_{eq} = C_1 + C_2 + C_3$$

24th January

Inductor

It is an electrical device /elements which stores energy in the form of magnetic field.


Series Combination

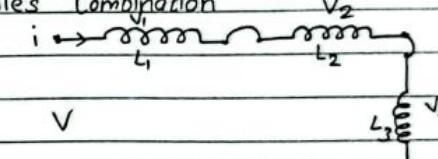

$$V = V_1 + V_2 + V_3$$

$$= L_1 \cdot \frac{di_1}{dt} + L_2 \cdot \frac{di_2}{dt} + L_3 \cdot \frac{di_3}{dt}$$

$$i = i_1 + i_2 + i_3$$

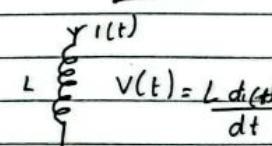


$$V = (L_1 + L_2 + L_3) \cdot \frac{di}{dt}$$

$$i(t) = \frac{1}{L} \int V(t) dt$$

$$L_{eq} = L_1 + L_2 + L_3$$

$$V = L_{eq} \cdot \frac{di}{dt}$$

Parallel Combination.

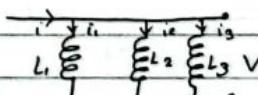

$$i = i_1 + i_2 + i_3$$

$$= \frac{1}{L_1} \int V dt + \frac{1}{L_2} \int V dt + \frac{1}{L_3} \int V(t) dt$$

$$i = \left(\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} \right) \int V \cdot dt$$

$$i_{\text{eq}} = \left(\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} \right) \int V \cdot dt$$

\checkmark


$$\frac{1}{L_{\text{eq}}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$

$$i = \frac{1}{L_{\text{eq}}} \int V(t)$$

X Kirchhoff's laws:

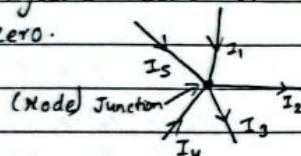a) Current law (KCL)

Algebraic sum of the current of at a junction is zero.



$$I_1 + I_5 + I_4 = I_2 + I_3$$

$$(I_1 + I_5 + I_4) - (I_2 + I_3) = 0$$

\checkmark $\sum I = 0$ at junction.


b) Voltage law (KVL).

Algebraic sum of the voltage or emf in a loop or mesh should be zero.


$$\epsilon_1 - V_1 + \epsilon_2 - V_2 + \epsilon_3 = 0$$

$$(\epsilon_1 + \epsilon_2 + \epsilon_3) = (V_1 + V_2)$$

\checkmark $\sum V = 0$ in mesh/loop.

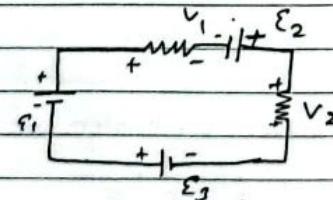

** Current Division

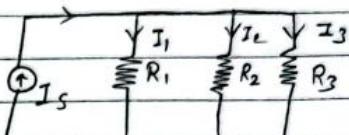


$$I_1 = \frac{1/R_1}{1/R_1 + 1/R_2 + 1/R_3} \times I_s$$

$$I_2 = \frac{1/R_2}{1/R_1 + 1/R_2 + 1/R_3} \times I_s$$

$$I_3 = \frac{1/R_3}{1/R_1 + 1/R_2 + 1/R_3} \times I_s$$

\checkmark $I_s = I_1 + I_2 + I_3$ KCL

** Voltage Division

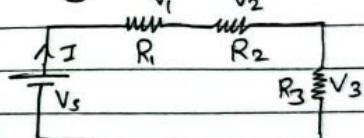

$$I = \frac{V_s}{R_{\text{eq}}} = \frac{V_s}{R_1 + R_2 + R_3}$$


$$V_1 = \frac{R_1}{R_1 + R_2 + R_3} \times V_s$$

$$V_2 = \frac{R_2}{R_1 + R_2 + R_3} \times V_s$$

$$V_3 = \frac{R_3}{R_1 + R_2 + R_3} \times V_s$$

\checkmark $V_s = V_1 + V_2 + V_3$ KVL.

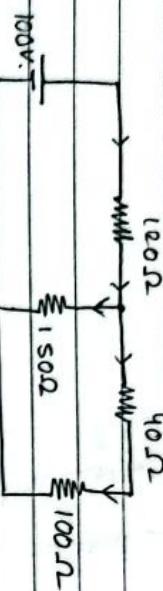Q. From the circuit, find the value of current through 100Ω .



$$R_{eq} = \left(\frac{140+100}{150} \right) \text{M}\Omega + 120$$

$$= \left(140/\text{M}\Omega \right) + 120$$

$$= \frac{140 \times 150}{140+150} + 120.$$

$$= 72.41 + 120$$

$$= 192.41 \Omega$$

$$I = \frac{V_s}{R_{eq}}$$

$$= \frac{140}{192.41}$$

$$= 0.51 \text{ A.}$$

$$I_1 = \frac{1}{150} \times 0.51$$

$$= \frac{1}{150} + \frac{1}{140}$$


$$\boxed{I_1 = 0.246 \text{ A}}$$

$$I_2 = I_s - I_1 \quad \boxed{I_2 = \frac{1/140}{1/150 + 1/140} \times 0.51}$$

$$= 0.51 - 0.246$$

$$= 0.27 \text{ A.} \quad \boxed{-0.265 \text{ A.}}$$

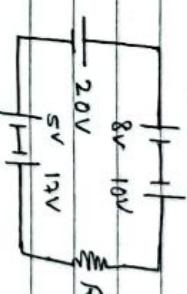Q. Find the voltage across R in the figure.




$$0.120 + 5 + 10 = 8 + VR + 12$$

$$0.135 = 25 + VR$$

$$\therefore VR = 10V$$

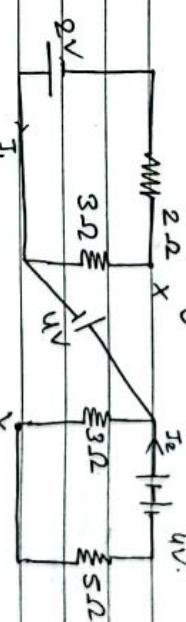Q. What is the difference in potential between points X and Y in the given circuit.



$$I_1 = \frac{2}{2+3} \quad I_2 = \frac{4}{3+5}$$

$$I_1 = \frac{2}{5} \quad I_2 = \frac{4}{8}$$

$$I_1 = 0.4 \text{ A.}$$

$$I_2 = 0.5 \text{ A.}$$

$$X \rightarrow 2\Omega \rightarrow 3\Omega \rightarrow Y$$

$$1.2V \quad 1.5V$$

$$V_x - 1.2 - 4 + 1.5 - V_y = 0$$

$$V_x - V_y = 1.2 + 4 - 1.5$$

$$\therefore V_x - V_y = 3.7 V$$

Application of Kirchhoff's law


a) Nodal Analysis

In nodal analysis we have to use KCL at junction or node.


Rules:

- Determine node in a circuit.
- Select a reference node among above nodes.
- Write down or name other node as unknown node voltage.

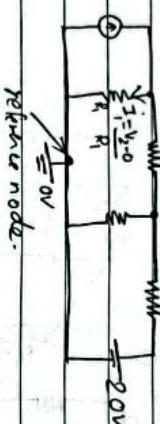4. Write down KCL equation at all unknown node



node voltage.

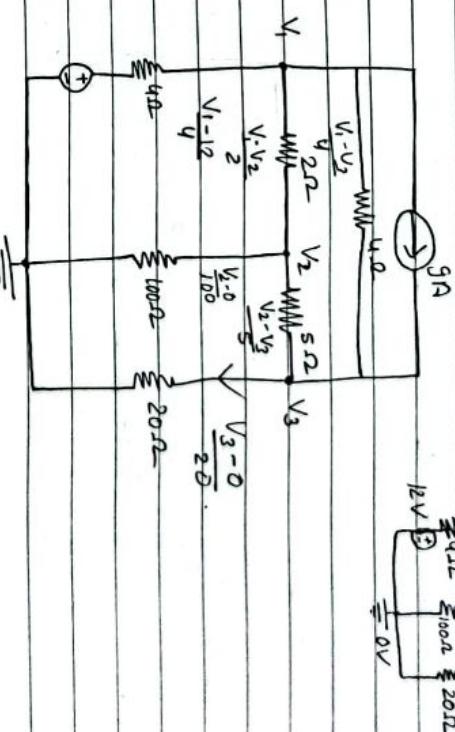

at Node 1 : (KCL)

$$\frac{V_1 - 12}{4} + \frac{V_1 - V_2}{2} + \frac{V_1 - V_3}{4} + 9 = 0$$

$$\left(\frac{1}{4} + \frac{1}{2} + \frac{1}{4} \right) V_1 - \frac{12}{4} - \frac{1}{2} V_2 - \frac{1}{4} V_3 + 9 = 0$$

$$\boxed{\frac{1}{4} V_1 - \frac{1}{2} V_2 - \frac{1}{4} V_3 = -6} \quad \dots \dots \dots \textcircled{1}$$

at Node 2 : (KCL)

$$\frac{V_1 - V_2}{2} = \frac{V_2}{100} + \frac{V_2 - V_3}{5}$$

$$\frac{1}{2} V_1 - \frac{V_2}{2} - \frac{V_2}{100} - \frac{V_2}{5} + \frac{V_3}{5} = 0$$

$$\frac{1}{2} V_1 - \left(\frac{1}{2} + \frac{1}{100} + \frac{1}{5} \right) V_2 + \frac{1}{5} V_3 = 0 \quad \textcircled{2}$$

Qn. Calculate the voltage across 5Ω resistor in the network given below using Nodal Analysis.



Date: Jan 25
Page: 1

Date: Jan 25
Page: 1

at Node 3:

$$\frac{V_2 - V_3}{S} + \frac{V_1 - V_2}{4} + 9 = \frac{V_3}{20}$$

$$\frac{V_2}{4} \left(\frac{1}{S} V_1 + \frac{1}{4} V_2 - \left(\frac{1}{S} + \frac{1}{4} + \frac{1}{20} \right) V_2 \right) = -9$$

$$\frac{1}{4} V_1 + \frac{1}{3} V_2 - \frac{1}{2} V_3 = -9 \quad \text{(iii)}$$

$$A \cdot x = b$$

$$\begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{4} \\ \frac{1}{2} & -\frac{7}{100} & \frac{1}{5} \\ \frac{1}{4} & \frac{1}{5} & -\frac{1}{2} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} -6 \\ 0 \\ -9 \end{bmatrix}$$

$$V_1 = 6.35V$$


$$V_2 = 11.76V$$

$$V_3 = 25.88V$$


$$I_2 = \frac{V_2 - V_3}{S} = \frac{11.76 - 25.88}{5} = -2.82 A$$

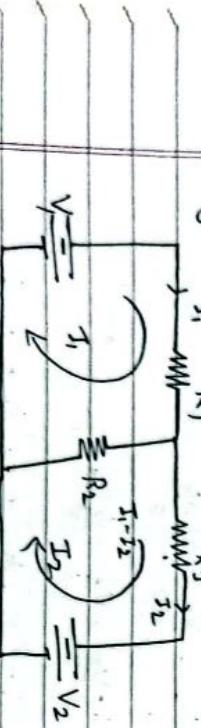b) Mesh Analysis.

It is used to just find current in the electric network using KVL equation in the mesh.



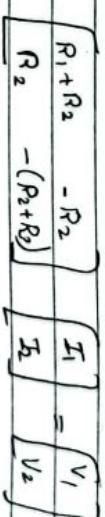Ques. Find the mesh current in each branch.



mesh-2 (kV)

$$(I_1 - I_2) R_2 - I_2 \cdot R_3 - V_2 = 0$$

$$(I_1 - I_2) R_2 - I_2 \cdot R_3 = V_2$$

$$\begin{bmatrix} R_1 + R_2 & -R_2 \\ R_2 & -(R_2 + R_3) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

mesh-2 (kV)

$$V_1 - I_1 R_1 - (I_1 - I_2) R_2 = 0$$

$$(R_1 + R_2) I_1 - R_2 I_2 = V_1$$

1) Finding mesh in the network.

2) Write down mesh current in each mesh in clockwise direction or anticlockwise direction.

3) Write down KVL equation in each mesh.

mesh-1:

$$\frac{U_1 I_1 - 10 I_2 + 10 (I_1 - I_2)}{30} = 12$$

mesh-2:

$$120 + I_1 30 = (I_2 - I_1) 10$$

$$50 I_2 + 10 I_2 - 10 I_1 = 60$$

$$120 = 10 I_2 - 10 I_1 - 30 I_1$$

$$50 I_2 + 10 I_2 - 10 I_1 = 60$$

$$120 = 10 I_2 + 20 I_1$$

$$-10 I_1 + 60 I_2 = 60$$

$$-40 I_1 + 10 I_2 = 120$$

$$-I_1 + 6 I_2 = 6$$

$$U_{011} - 10 I_2 = -120$$

$$I_1 = 2.86 A$$

$$50 I_2 + 60 + 10 (I_2 + I_1) = 0$$

$$60 I_2 + 10 I_1 = -60$$


$$I_2 = 0.52 A$$

$$24 I_1 - 72 - 12 = -12$$

$$23 I_1 = 66$$

$$I_1 = 3 A$$

Q.

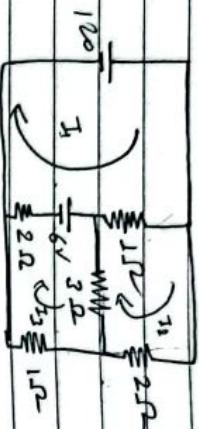

mesh - 1

$$120 = (I_1 - I_2)1 + 6 + (I_1 - I_3) \cdot 2$$

$$120 = 3I_1 - I_2 + 6 - 2I_3 \quad \text{.....(i)}$$

$$3I_1 - I_2 - 2I_3 = 114 \quad \text{.....(i)}$$

mesh - 2

$$(I_1 - I_2)1 + (I_2 - I_3)3 = 2I_2$$

$$I_1 - 6I_2 + 2I_3 = 0 \quad \text{.....(ii)}$$

mesh - 3

$$6 + (I_1 - I_2)2 = 3(I_3 - I_2) + I_3$$

$$6 = 2I_1 - 3I_2 + 6I_3$$

$$-2I_1 - 3I_2 + 6I_3 = 6 \quad \text{.....(iii)}$$

Matrix:

$$\begin{bmatrix} 3 & -1 & 2 \\ 1 & -6 & 3 \\ -2 & -3 & 6 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 114 \\ 0 \\ 6 \end{bmatrix}$$

$$I_1 =$$

$$I_2 =$$

$$I_3 =$$

induction.

$$E_{max} = B \cdot l \cdot v, \theta = 90^\circ$$



$$E_{max} = B \cdot l \cdot v \cdot 0, \theta = 0^\circ$$

It is Based on Faraday's law of electromagnetic induction.

X Introduction to AC Circuits and parameters:

Rotary electro mechanical generators produce voltage alternating in polarity and reversing positive and negative over time.

Either as a voltage switching polarity or as a current switching direction back and forth, this kind of electricity is known as Alternating current (AC).

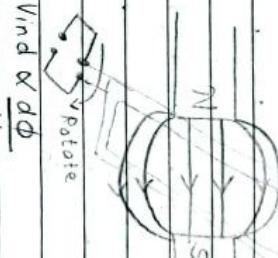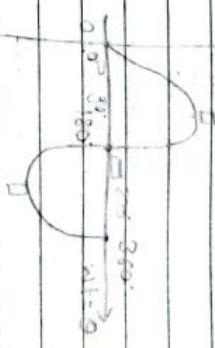Wind $\propto \frac{d\phi}{dt}$ 

In the presence of magnetic field when we rotate a coil an emf (voltage) is induced in the coil which is directly proportional to the rate of change of flux.

From graph,

$E_{emf} = B \cdot l \cdot \sin \theta$ where, B =Magnetic field density (Tesla)

l =Length of conductor.

v =Velocity

θ =angle of rotation.


Symbol :



XX AC waveform:

When an alternator produces AC voltage the voltage switches polarity over time. When graphed over time the current is traced.

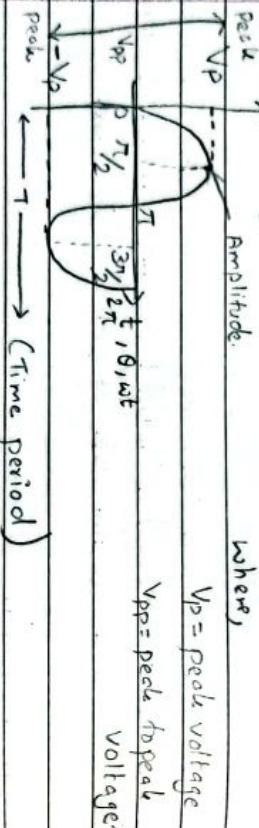The shape is obtained by plotting the instantaneous values of an alternating quantity such as voltage or current along the y-axis and time(t) along the x-axis is called wave form.



where,

V_p = Peak voltage


V_{pp} = peak to peak voltage

- ### XX Frequency:
- The cycle per second is known as frequency.
 $f = \text{cycle/sec}$, unit = Hz
- ### XX Time Period:
- Time taken in seconds by voltage or a current to complete one cycle is called time period.
- ### XX Average value of a waveform:
- The average value of waveform can be found for any wave like sinusoidal, triangular, trapezoidal square or other shape
- The average value of a cycle of a waveform is the area under the waveform divided by the length one cycle i.e.
- $$V_{avg} = \frac{1}{T} \int_0^T V(t) dt$$

XX Amplitude:

The maximum positive or negative value obtained by alternating quantity in one complete cycle is called amplitude or peak value.

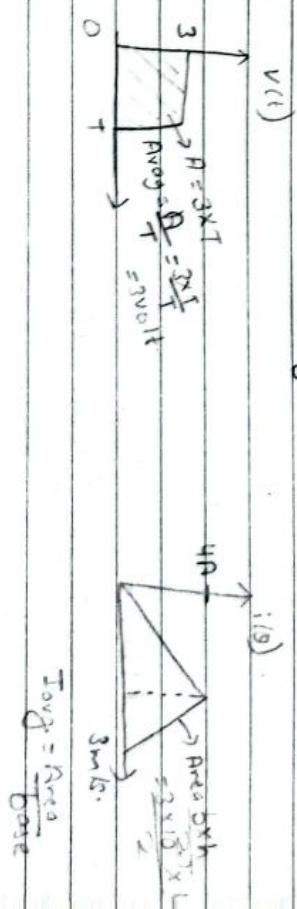
The maximum value of voltage or current is represented by E_m or V_m or V_p and I_m or I_p respectively.



$$\frac{2 \times 4.1 \times 10^{-3}}{2} = \frac{-3 \times 10^{-3} \times 4}{2} \\ = 2 \times 10^{-3}$$

Single phase AC Circuit.

With Resistor

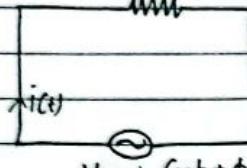

$$\bar{I} = \frac{V_m < \phi}{Z_R}$$

$$\bar{I} = \frac{V_m}{Z_R} < \phi$$


$$\bar{I} = I_m < \phi$$

↓ phasor form

$$Z_R = R$$


$$\therefore I_m = V_m$$

$$|Z_R|$$

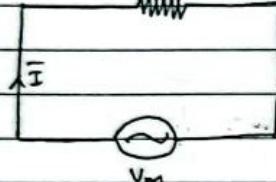

In resistor current and voltage are in same phaset.

With capacitance

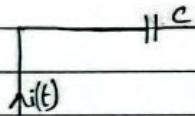


$$\bar{I} = \frac{V_m < \phi}{Z_C}$$

$$= \frac{V_m < \phi}{-j \frac{1}{\omega C}}$$

↓ phasor form.

$$Z_C = \frac{1}{j\omega C} = -j \frac{1}{\omega C}$$


$$= \frac{V_m < \phi}{|\frac{1}{\omega C}|} < -90^\circ$$

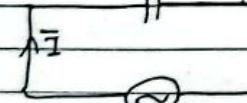


$$\bar{I} = \frac{V_m}{|\frac{1}{\omega C}|} < +90^\circ$$

In capacitor current leads voltage by 90°.

With inductor

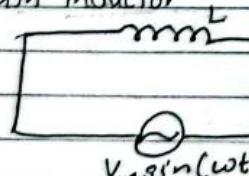

phasor form

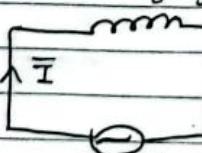

$$Z_L = jX_L = j\omega L$$

$$\bar{I} = \frac{V_m < 0}{Z_L}$$

$$= \frac{V_m < 0}{j\omega L}$$

$$= \frac{V_m < 0}{(\omega L) < 90^\circ}$$

$$\bar{I} = \frac{V_m}{(\omega L)} < -90^\circ$$

$$= |(\omega L)|$$

In inductor current lags voltage by -90°.

Imaginary


$$Z_L = j\omega L$$

Real

$$Z_R = R$$


$$Z_C = -j \frac{1}{\omega C}$$

Impedance of different Elements.

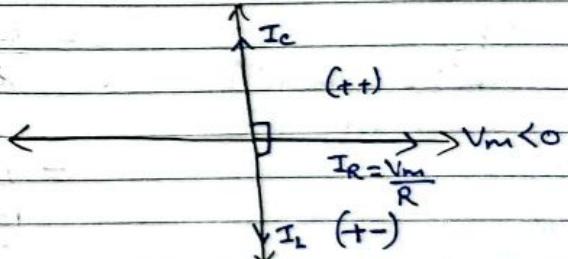

phasor

form

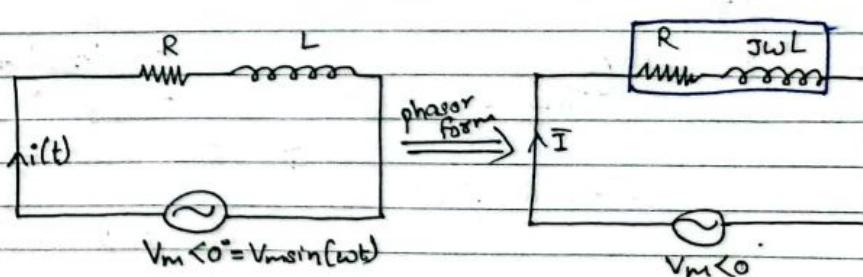

w Series RLC circuit
 $Z_T = \frac{R}{R+i\omega L} + \frac{1}{i\omega C}$

$$Z_T = R + i\omega L \rightarrow |Z_T| = \sqrt{R^2 + (\omega L)^2}$$
 $\angle Z_T = \phi = \tan^{-1}\left(\frac{\omega L}{R}\right)$


$$\bar{I} = V_m < 0$$

$$\bar{I} = \frac{V_m < 0}{Z_T}$$

$$(i\omega L) \therefore (R, i\omega L)$$

$$R + i\omega L$$
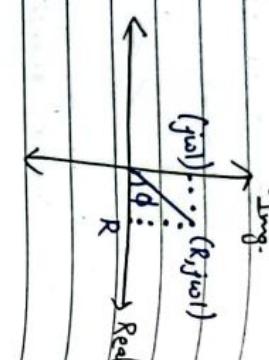
$$= \frac{V_m < 0}{\sqrt{R^2 + (\omega L)^2}} \angle \tan^{-1}\left(\frac{\omega L}{R}\right)$$



series.


$$Z_T = Z_R + Z_L + Z_C$$

$$\frac{1}{Z_{eq}} = \frac{1}{Z_R} + \frac{1}{Z_L} + \frac{1}{Z_C}$$

$$Z_T = R + i\omega L - j\frac{1}{\omega C}$$

$$Z_T = \frac{R + j\left(\omega L - \frac{1}{\omega C}\right)}{Real + Imaginary}$$

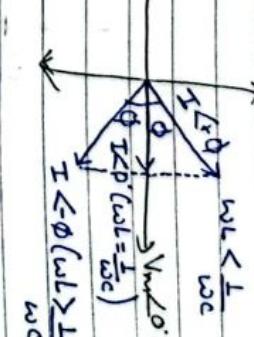if $\omega L \gg \frac{1}{\omega C}$ \Rightarrow inductor



if $\omega L < \frac{1}{\omega C}$ \Rightarrow capacitance.

$$Power = V_{rms} \cdot I_{rms} \cdot \cos \phi$$

+ $\tan^{-1}\left(\frac{1}{\omega LC}\right)$

power factor

A 200V, 50Hz AC supply is applied to a coil of

0.08H inductance and 4Ω resistance connected in series with the capacitor of 8μF. Calculate.


i) Independence

ii) Circuit current

iii) phase angle between current and voltage

iv) power factor

v) Voltage across each element.

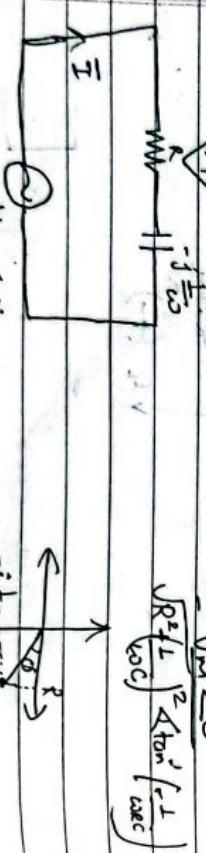

$$Vm < 0 \quad \text{phaser form}$$

$$= \frac{V_m < 0}{Z_T}$$

$$V_m < 0 = V_{rms} \sin(\omega t)$$

$$\bar{I} = \frac{V_m < 0}{R - j\frac{1}{\omega C}}$$

$$= \frac{V_m < 0}{R + j\omega L}$$

$$= \frac{V_m < 0}{\sqrt{R^2 + (\omega L)^2}} \angle \tan^{-1}\left(\frac{\omega L}{R}\right)$$

$$Z_T = R - j\frac{1}{\omega C} \rightarrow \angle Z_T = \phi = \tan^{-1}\left(\frac{1}{\omega RC}\right)$$

Soln:- here, $\frac{4.5}{0.08} = 56.25 \text{ A}$

$$= \frac{0.08 \times 8 \times 10^{-6}}{56.25} = 0.0000144 \text{ pF}$$

v. $\bar{V}_L = \bar{I} \cdot \bar{R}$
 $= 0.643 \angle 89.385^\circ \times 4$
 $= 2.572 \angle 89.385^\circ$

$$\bar{V}_L = \bar{I} \times \bar{Z}$$

$$= 0.643 \angle 89.385^\circ \times 25.12j^\circ$$

$$V_L = 16.15 \angle 179.385^\circ$$

$$\bar{V}_C = \bar{I} \times \bar{Z}_C$$

$$\begin{aligned} Z_C &= j\omega C = j \cdot (2\pi 50) \times 0.08 = 25.12j^\circ \\ Z_C &= -j \frac{1}{(2\pi 50 \times 8 \times 10^{-6})} = -398.089j^\circ \end{aligned}$$

$$Z_T = 4 + 25.12j - 398.089j^\circ$$

$$Z_T = 4 - 372.969j^\circ$$


$$i) \bar{I} = V \angle 0$$

$$Z_T$$

$$= 4 - 372.969j^\circ$$

$$= 4 - 372.969j^\circ$$

$$= 4 - 372.969j^\circ$$

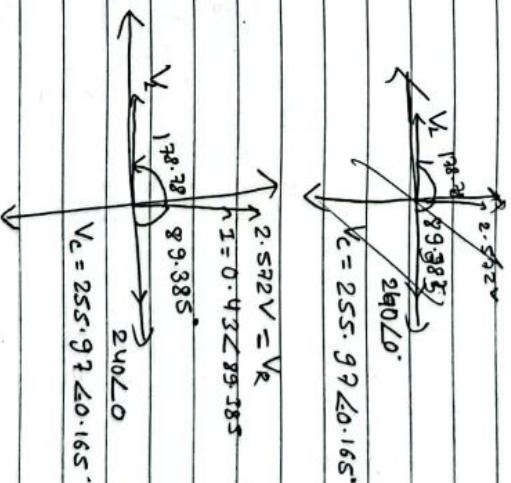

$$\begin{aligned} I &= 0.432 \angle 29.385^\circ \\ 2.572V &= V_R \\ 2.572 &= V_R \end{aligned}$$

$$\begin{aligned} 179.385^\circ &= 89.385^\circ \\ 240 &= 240 \end{aligned}$$

$$V_C = 255.97 \angle 0.165^\circ$$

$$iii)$$

$$\phi = 89.385^\circ$$

$$\downarrow \phi 89.385^\circ (\text{lead})$$

$$iv. \text{ power factor (p.f)} = \cos \phi$$

$$= \cos (89.385^\circ)$$

$$= 0.0107.$$

Different types of power

a. Real power or Active power. (P). \rightarrow Watt.

$$V_{rms} \times I_{rms} \times \cos \phi = P$$

power factor.

b. Reaching power (g) → VAR

join

$$\Rightarrow \phi = V_{rms} I_{rms} \cdot \sin \phi$$

c. Apparent Power (S) \longrightarrow (VA)

$$S = P_+ j \phi = V_{\text{max}} \cdot T_{\text{rm}}$$

$$|S| = \sqrt{P^2 + Q^2}$$

$$S = (p+q) \cdot \frac{1}{2} \cdot \sin(\theta)$$

$$S = (P+Q)$$

$$IS = \sqrt{P^2 + Q^2}$$

$\beta_1 = \beta$

$$P = |\vec{S}| \cos \phi$$

$$p = |S| \cos \phi$$

Digitized by srujanika@gmail.com

In the network shown in figure determine:

- Total impedance
- The current
- The current in each phase
- The overall power factor.
- Volt ampers, active power of reactive power

(5) 230.50kV

$Z_1 = 5 + j\omega(0.01)$

$= 5 + j(2\pi f \times 0.01)$

$= 5 + j(2\pi 50 \times 0.01)$

$= 5 + j\pi$

$\therefore Z_1 = 5 + 3.14j$

$Z_2 = 7 + j\omega(0.015)$

$= 7 + j(2\pi f \times 0.015)$


$= 7 + j(2\pi 50 \times 0.015)$

$\therefore Z_2 = 7 + 4.71j$

$Z_3 = 12 - j \frac{1}{(2\pi \times 50 \times 180 \times 10^{-6})}$

$= 12 - j17.69$

$\therefore Z_g = 12 - j17.69j$

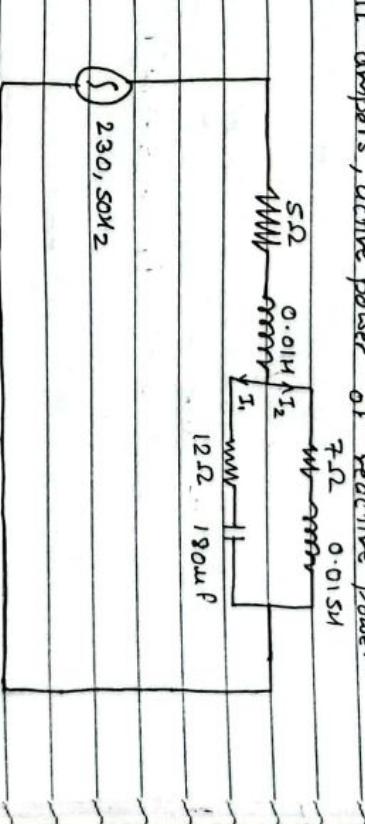

$$Z_{eq} = (Z_1/Z_2) + Z_3$$

$$= \frac{Z_1 \times Z_2}{Z_1 + Z_2} + Z_3$$

$$= (4+3j) \times \frac{(4-16j)}{(4+3j) + (4-16j)} = (4+3j) + (2+8j)$$

$$= 1.40 + 4.42j + 2+8j$$

~~$$= 20\angle 26^\circ$$~~

$$I_1 = \frac{Z_2}{Z_1 + Z_2} \times 25 < 0$$

$$= \frac{(4-16j)}{(4+3j) + (4-16j)} \times 25 < 0$$

$$= 20 < -36.86 \text{ Amp}$$

Neutral

$$I_2 = \frac{Z_1}{Z_1 + Z_2} \times 25 < 0$$

$$= \frac{4+3j}{(4+3j) + (4-16j)} \times 25 < 0$$

$$= 15 < 53.13 \text{ Amp}$$

$$V = I \cdot Z_{eq}$$

$$= 25 < 0^\circ \times (6+8j)$$

$$= 250 < 53.13$$

$$J = (53.13 - 0^\circ) = 53.13^\circ \text{ (lagging)}$$

$$P \cdot f = \cos \phi$$



$$= \cos(53.13^\circ)$$

$$P \cdot f = 0.60$$

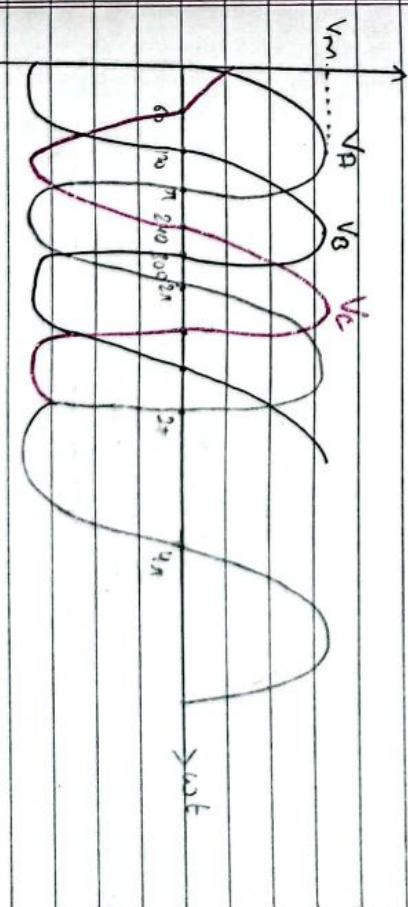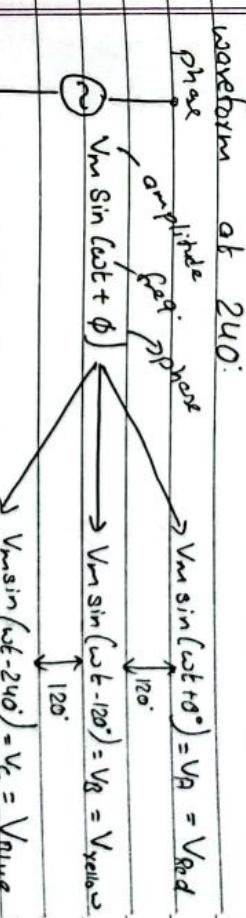1.8 Three Phase AC Circuit Analysis.

→ A three phase supply is a set of three alternating quantities displaced from each other by an angle of 120° . A three phase voltage is shown below.

It consists of three phases - phase A, phase B and phase C. Phase A waveform starts at 0° and phase B waveform starts at 120° and phase C waveform at 240° :



Time waveform



$$V_m < \dots \rightarrow V_m < 240^\circ = V_C$$

$$\rightarrow V_m < 0^\circ = V_A$$


$$V_B = V_m < -120^\circ$$

fig: phasor Representation

Generation of 3- ϕ system:

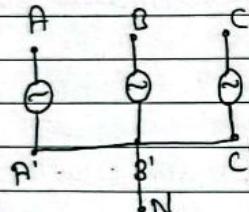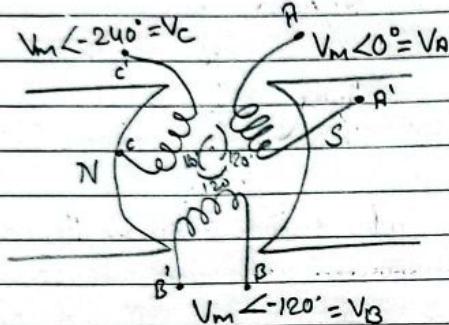


star-Wye connection

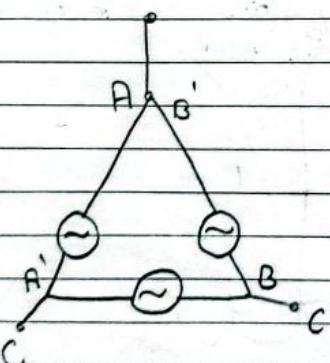

star-Delta/Ring connection.

Advantages of 3- ϕ system:

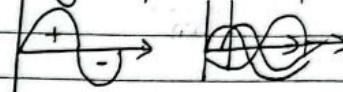→ Three phase system supplies constant voltage whereas single phase is pulse setting waveform.




→ The magnitude of 3- ϕ system is 1.5 times higher than 1- ϕ system.

$$V_m \rightarrow 1.5 V_m$$


$$1-\phi \quad 3-\phi$$

$$P = V_m I_m$$

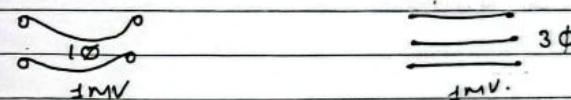
→ Weight of the copper in 3- ϕ system is $(\frac{3}{4})^{th}$ time of 1- ϕ .



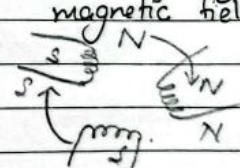
→ 3- ϕ produces rotating magnetic field whereas 1- ϕ alternating magnetic field.



Balanced Supply

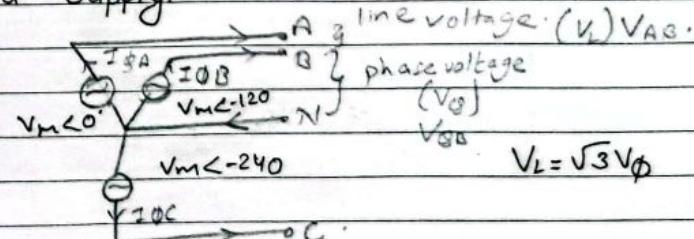

star-connection

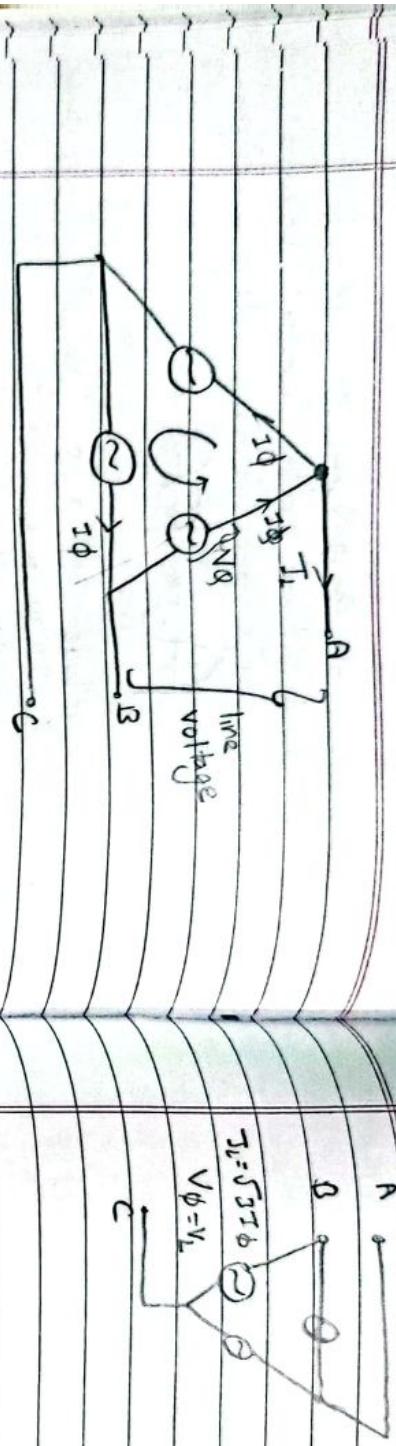


$$V_\phi = V_{\text{line}}$$

$$I_L = \sqrt{3} I_\phi$$

17 Feb.

Three phase balanced load

a. Start Connection

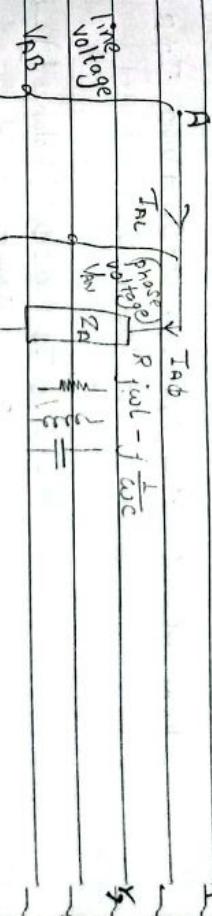

$$V_{BC}$$

$$V_{AC}$$

$$V_{AB} = I_\phi Z$$

$$I_{LA} = I_{\phi A}$$

$$I_{LC} = I_{\phi C}$$

$$\text{if } Z_A = Z_B = Z_C \text{ (balanced load)}$$



$$\text{line } V_{AB} = V_{AN} - V_{BN} \quad \text{phase } V_{AB}$$

$$V_{AC} = V_{AN} - V_{CN} \quad \text{phase } V_{AC}$$

$$V_{BC} = V_{BN} - V_{CN} \quad \text{phase } V_{BC}$$

b. Delta Connection.

$$I_{\Phi A} = \frac{V_{\Phi A}}{Z_A} = \frac{V_{AN}}{Z_n}$$

$$I_{\Phi B} = \frac{V_{\Phi B}}{Z_B} = \frac{V_{BN}}{Z_n}$$

$$I_{\Phi C} = \frac{V_{\Phi C}}{Z_C} = \frac{V_{CN}}{Z_n}$$

$$\therefore I_N = I_{\Phi A} + I_{\Phi B} + I_{\Phi C} = I_{LA} + I_{LB} + I_{LC}$$

if $I_N = 0$ (Balanced load).

Power:

$$\text{Real power} \cdot P = V_{\Phi A} \cdot I_{\Phi A} \cdot \cos \theta_A + V_{\Phi B} \cdot I_{\Phi B} \cdot \cos \theta_B$$

$$+ V_{\Phi C} \cdot I_{\Phi C} \cdot \cos \theta_C$$

$$P = 3V\phi \cdot I\phi \cdot \cos \phi \quad (\text{balanced}) \rightarrow \text{watt.}$$

$$= \frac{\sqrt{3}}{\sqrt{3}} \cdot V_L \cdot I_L \cdot \cos \phi$$

$$P = \sqrt{3} \cdot V_L \cdot I_L \cdot \cos \phi$$

$$V_{AB} = V_{\Phi A}$$

$$V_{BC} = V_{\Phi B}$$

$$V_{AC} = V_{\Phi C}$$

$$\rightarrow \text{line voltage} = \text{phase voltage}$$

$$\text{Reactive Power } (Q) \\ Q = \sqrt{3}V\phi \cdot I\phi \sin \phi = \sqrt{3} \cdot V_L \cdot I_L \cdot \sin \phi$$


$$V_L = V\phi \quad (\text{Balanced})$$

$$I_L = \sqrt{3} I\phi$$

Apparent Power (S)

$$S = \sqrt{3} \cdot V\phi \cdot I\phi = \sqrt{3} \cdot V_L \cdot I_L$$
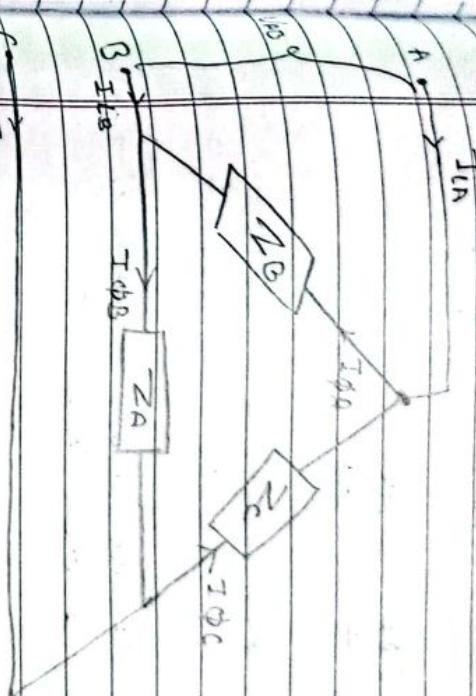
$$S = P + jQ \\ \underline{\text{---}} \quad \underline{\text{---}} \quad \underline{\text{---}} \\ \underline{\text{---}} \quad \underline{\text{---}} \quad \underline{\text{---}}$$



$$I_{\Phi A} + I_{\Phi C} = I_{\Phi B}$$

$$\text{if } I_{\Phi A} = I_{\Phi B} - I_{\Phi C} \quad \text{phase current}$$

$$I_{\Phi C} = I_{\Phi B} - I_{\Phi A}$$

$$\text{if } Z_A = Z_B = Z_C \quad (\text{Balanced load})$$

$$Z_A \neq Z_B \neq Z_C \quad (\text{Unbalanced load})$$

$$I_{\Phi A} = \frac{V_{\Phi A}}{Z_A} = \frac{V_{AN}}{Z_n}$$

$$I_{\phi B} = \frac{V_{\phi c}}{Z_B} = \frac{V_{\phi c}}{Z_0}$$

$$I_{\phi C} = \frac{V_{\phi c}}{Z_C} = \frac{V_{\phi c}}{Z_0}$$

$$\text{Real Power (P)} = V_{\phi A} \cdot I_{\phi A} \cdot \cos\theta_A + V_{\phi B} \cdot I_{\phi B} \cdot \cos\theta_B + V_{\phi C} \cdot I_{\phi C} \cdot \cos\theta_C$$

$$P = 3V_{\phi} \cdot I_{\phi} \cdot \cos\phi \quad (\text{balanced}) \rightarrow \omega \text{ at.}$$

$$= 3 \cdot \frac{I}{\sqrt{3}} \cdot V_L \cdot I_L \cdot \cos\phi$$

$$P = \sqrt{3} V_L I_L \cos\phi$$

Reactive power (Q)

$$Q = 3V_{\phi} \cdot I_{\phi} \sin\phi = \sqrt{3} V_L \cdot I_L \cdot \sin\phi$$

Apparent Power (S)

$$S = 3 \cdot V_{\phi} I_{\phi} = \sqrt{3} V_L I_L$$

$$S = P + jQ.$$

$$\left. \begin{aligned} I_{\phi B} &= \frac{V_{\phi B}}{Z_B} = \frac{400 \angle -120^\circ}{25+j40} \\ I_{\phi C} &= \frac{V_{\phi C}}{Z_C} = \frac{400 \angle -240^\circ}{25+j40} \end{aligned} \right\} \quad \text{Ans}$$

$$\left. \begin{aligned} I_{\phi B} &= \frac{V_{\phi B}}{Z_B} = \frac{400 \angle -120^\circ}{25+j40} \\ I_{\phi C} &= \frac{V_{\phi C}}{Z_C} = \frac{400 \angle -240^\circ}{25+j40} \end{aligned} \right\} \quad \text{Ans}$$

- g. A balanced 3- ϕ delta connected load has phase impedance of $(25+j40)\Omega$. If $400V$, 3ϕ supply is connected to this load. find.
- i) Phase current
 - ii) Power supplied to the load.
 - iii) Reactive of apparent power.

Ans :- here

classmate
Date _____
Page _____

classmate
Date _____
Page _____

Three Phase AC system.


$$\begin{aligned} \phi &= 0^\circ - (-57.98^\circ) = 57.98^\circ \text{ (lagging)} \\ \dot{q} &= -100 - (177.99) = 59.38 \end{aligned}$$

$$\begin{aligned} p.f. &= \cos \phi = (\cos 57.98^\circ) \\ &= 0.53. \end{aligned}$$

$$\begin{aligned} P &= 3V\phi \cdot I\phi \cdot \cos \phi \\ &= 3 \times 400 \cdot 8.47 \cdot 0.53 \\ &= 5386.92 \text{ watt} \end{aligned}$$

$$\begin{aligned} Q &= 3 \cdot V\phi \cdot I\phi \cdot \sin \phi = 3 \cdot 400 \cdot 8.47 \cdot \sqrt{X_{\text{series}}} \cdot X_{\text{series}} \\ &= 8619.68 \text{ VAR} \end{aligned}$$
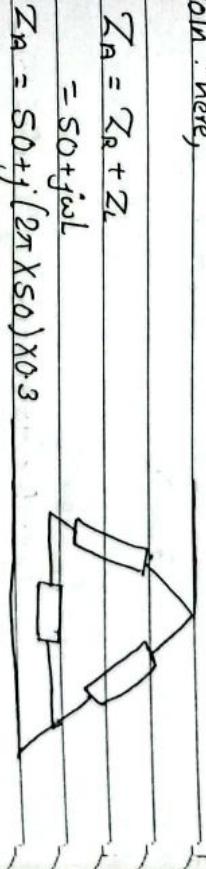
$$\begin{aligned} S &= 3V\phi \cdot I\phi \\ &= 10164 \text{ VA} \end{aligned}$$



John :- here,

$$\begin{aligned} Z_A &= Z_R + Z_L \\ &= 50 + j10 \end{aligned}$$

$$Z_R = 50 + j(2\pi \times 50) \times 0.3$$

$$Z_R = 50 + 30\pi j = Z_R = Z_L$$

$$V_{\phi B} = 415 < 0^\circ = V_{\phi A}$$

$$V_{\phi C} = 415 < -120^\circ = V_{\phi B}$$

$$V_{\phi C} = 415 < +120^\circ = V_{\phi C}$$

$$I_{\phi A} = \frac{V_{\phi A}}{Z_R} = \frac{415 < 0^\circ}{50 + 30\pi j} = 3.88 < -62.05^\circ$$

$$I_{\phi B} = \frac{V_{\phi B}}{Z_R} = \frac{415 < -120^\circ}{50 + 30\pi j} = 3.88 < 177.95^\circ$$

$$I_{\phi C} = \frac{V_{\phi C}}{Z_R} = \frac{415 < +120^\circ}{50 + 30\pi j} = 3.88 < 57.95^\circ$$

$$6.72 < -92.05^\circ$$

$$\begin{aligned} I_{\phi A} &= I_{\phi A} - I_{\phi C} = 3.88 < -62.05^\circ - 3.88 < 57.95^\circ \\ I_{\phi B} &= I_{\phi B} - I_{\phi A} = 6.72 < +177.95^\circ \\ I_{\phi C} &= I_{\phi C} - I_{\phi A} = 6.72 < 27.95^\circ \end{aligned}$$

$$P_A = V_{\Phi A} \cdot I_{\Phi A} \cdot \cos \phi_A$$

$$= 415 \times 3.88 \cos(0 - (-62.05))$$

$$= 754.70$$

$$P_B = V_{\Phi B} \cdot I_{\Phi B} \cdot \cos \phi_B$$

$$= 415 \times 3.88 \cos(-120 - (-27.95))$$

$$= -1531.88 \angle 754.70$$

$$P_C = V_{\Phi C} \cdot I_{\Phi C} \cdot \cos \phi_C$$

$$= 415 \times 3.88 \cos(120 - 57.95)$$

$$= 754.70$$

$$P_T = P_A + P_B + P_C$$

$$= 754.70 + (-1531.88) + 754.70 + 754.70$$

$$= -2244.2264 + 10$$

$$V_{\Phi A} = \frac{100}{\sqrt{3}} \angle 0^\circ$$

$$V_{\Phi B} = \frac{100}{\sqrt{3}} \angle -120^\circ$$

$$V_{\Phi C} = \frac{100}{\sqrt{3}} \angle +120^\circ$$

$$I_{\Phi A} = I_{\Phi B} = \frac{100\sqrt{3} \angle 0^\circ}{8+6.28j} = 5.70 \angle -37.28^\circ$$

$$I_{\Phi C} = I_{\Phi B} = \frac{100\sqrt{3} \angle -120^\circ}{8+6.28j} = 5.70 \angle -157.28^\circ$$

$$I_{\Phi A} = 3.88 \angle -62.05^\circ$$

$$415 \angle -120^\circ = V_{\Phi B}$$

$$V_{\Phi A}$$

$$P_A = V_{\Phi A} \cdot I_{\Phi A} \cdot \cos \phi$$

$$= \frac{100}{\sqrt{3}} \times 5.70 \cdot \cos(0 - (-62.05)) = 260.10 \text{ Watt.}$$

$$P_B = V_{\Phi B} \cdot I_{\Phi B} \cdot \cos \phi$$

$$= \frac{100}{\sqrt{3}} \times 5.70 \cdot \cos(-120 - (-157.28)) = 260.10 \text{ Watt.}$$

A $3-\Phi$ load consist of three similar inductive coil each of resistance of 8Ω and inductance $20mH$.


The supply voltage is $100V$. $50Hz$. Calculate the line current, total power consumed by load in the star connection. And Draw the phasor Diagram.

\rightarrow soln: here,

$$Z_A = Z_B = Z_C$$

$$= 8 + j(2\pi 50) \times 20 \times 10^{-3}$$

$$= 8 + 6.283j$$

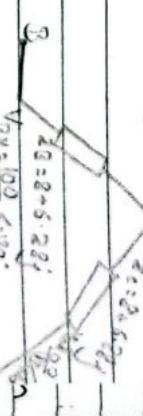


$$\begin{aligned}P_c &= V_{\phi c} \cdot I_{\phi c} \cdot \cos \phi \\&= \frac{100}{\sqrt{3}} \times 5.70 \times \cos(120 - 82.21) \\&= 260.06 \text{ watt.}\end{aligned}$$

$$\begin{aligned}Q_A &= V_{\phi A} \cdot I_{\phi A} \cdot \sin \phi_A \\&= 203.61 \text{ VAR}\end{aligned}$$


$$\begin{aligned}S &= P_A + j Q_A \\&= 260.1 + 203.61 j\end{aligned}$$

ELECTRICAL MACHINES

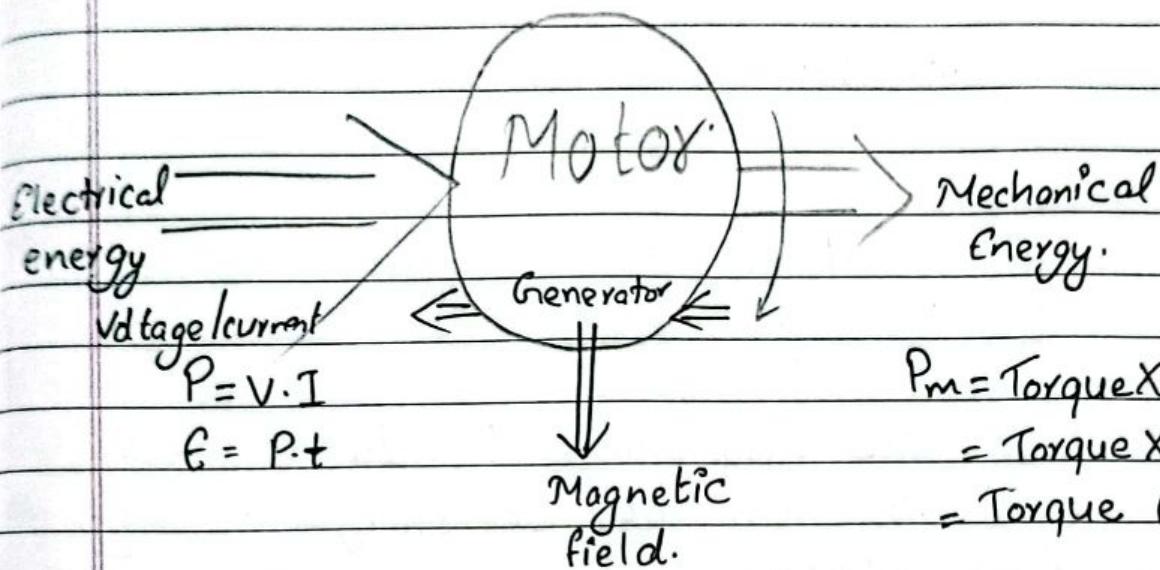

$$\begin{aligned}
 P_m &= \text{Torque} \times \omega \\
 &= \text{Torque} \times (2\pi n) \\
 &= \text{Torque} \frac{(2\pi N)}{60}
 \end{aligned}$$

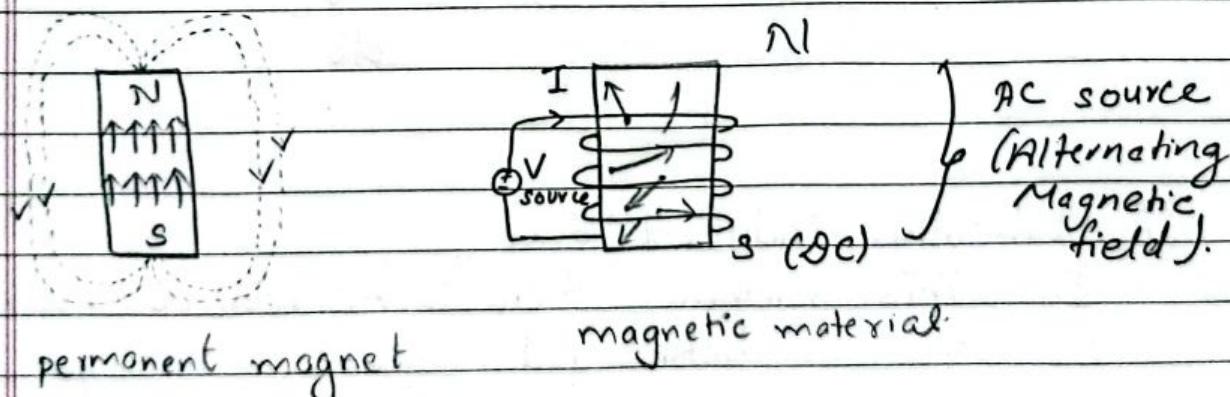Magnetic field : Magnetic Field is the phenomenon by which energy is converted from one form to another form in Motor, Generator, Transformer.




* Faraday's law

In 1821 A.D, Micheal Faraday, formulated the basic two laws underlying the phenomenon of electromagnetic induction.

Those two laws are :-


1st law : Whenever the magnitude of magnetic flux linking with a coil changes w.r.t

time an emf will be induced in the coil.

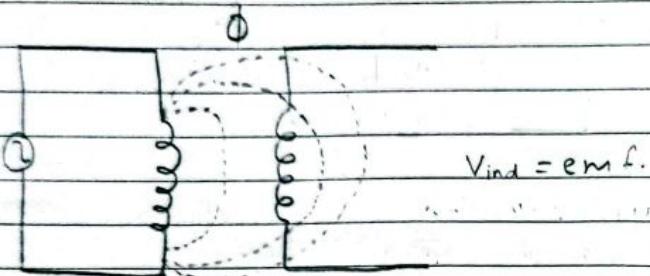

2nd law: The magnitude of induced emf is equal to the rate of change of magnetic flux linkage:
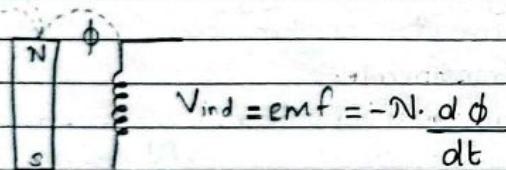
$$\text{i.e. } \text{emf} = \text{Vind} = -N \frac{d\phi}{dt}$$



i. Statically induced emf

In this method there is no relative motion between conductor and magnet.


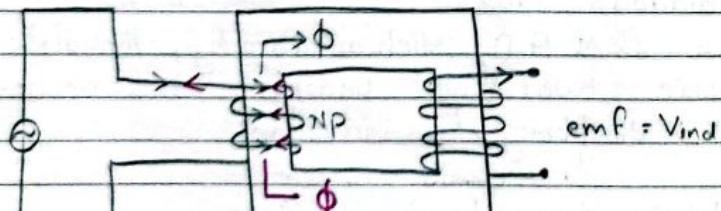


fig. Transformer

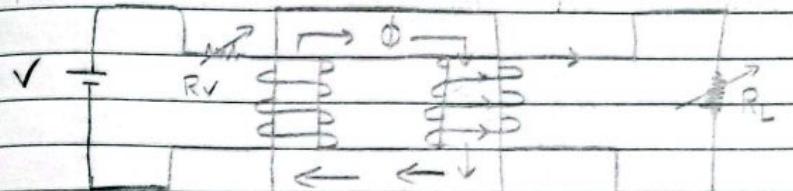


The direction of statically induced emf is given by Lenz's law.

"According to Lenz's law, the statically induced emf will drive the current in such a direction that the magnetic flux due to the induced current will oppose the cause by which emf was induced."

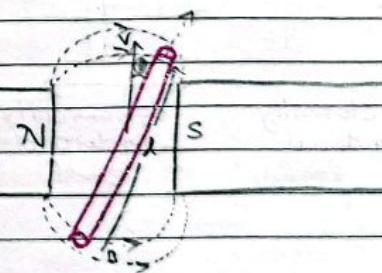ii) Dynamic induced emf.

In this method there is relative motion between the conductor and the magnet.



$$\text{Emf} = \text{Vind} = B \cdot l \cdot V \sin \theta$$

$$\theta = 90^\circ$$


$$\text{Vind (max)} = B \cdot l \cdot V$$

where, B = magnetic field density

l = length of coil

V = relative velocity of coil.

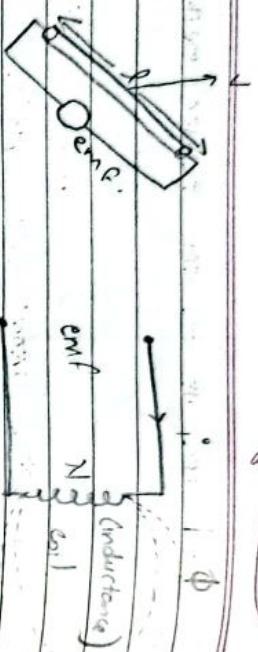and used to transfer power between two circuits by mutual induction.



$$L = N \cdot \Phi, \text{ unit Henry}$$

Now,

$$N \cdot \Phi = L \cdot i$$

Dif both side w.r.t time.

$$\frac{d(N \cdot \Phi)}{dt} = \frac{d(L \cdot i)}{dt}$$

$$N \cdot \frac{d\Phi}{dt} = L \cdot \frac{di}{dt} + i \cdot \frac{dL}{dt}$$


$$\text{emf} = L \cdot \frac{di}{dt} + i \cdot \frac{dL}{dt}$$

statically induced
dynamic induced


29 Feb, 2024

Transformer

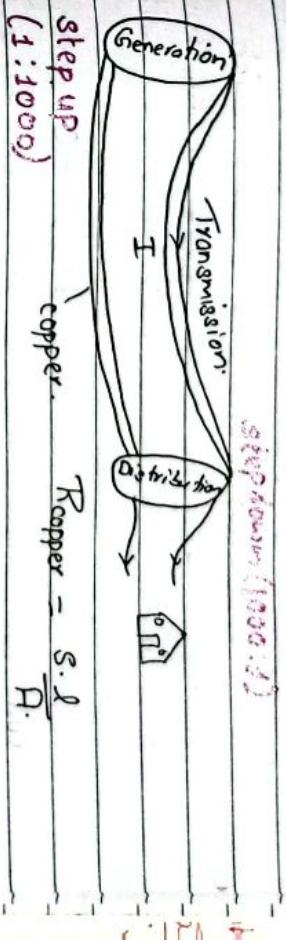A transformer is a device which is used to step-up voltage than that of generating voltage to achieve economical transmission and to step-down those dangerous high voltage level to suitable standard voltages to achieve safety distribution, it is static device



Construction

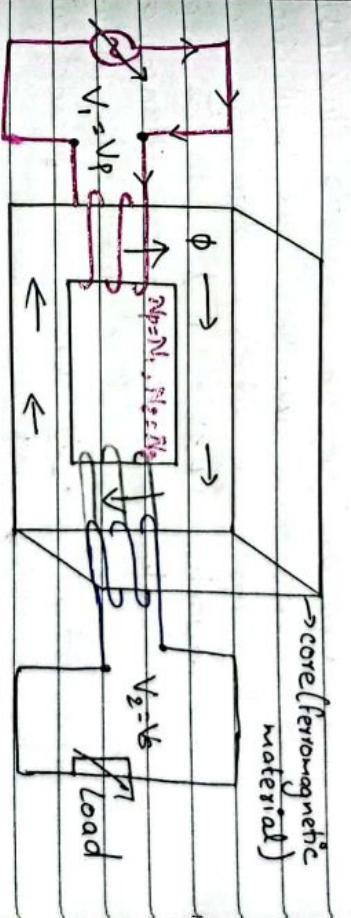

Primary coil ($N_1 = N_p$)
 Secondary coil ($N_2 = N_s$)

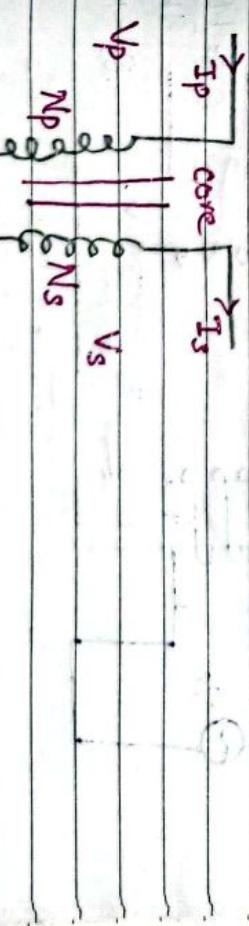



Fig: Symbol of Transformer.

Working principle and emf equation of transformer

Basically a transformer consists of a ferromagnetic core and two separated coils which are wound in the two limbs of the core. The coils made of copper and insulated with insulating materials.

When the coil is supplied by AC voltage the coil will draw some current (I_1), let us assume that the coil is purely inductive. Hence current lags the voltage by 90°. The wave form of voltage and current are shown below.

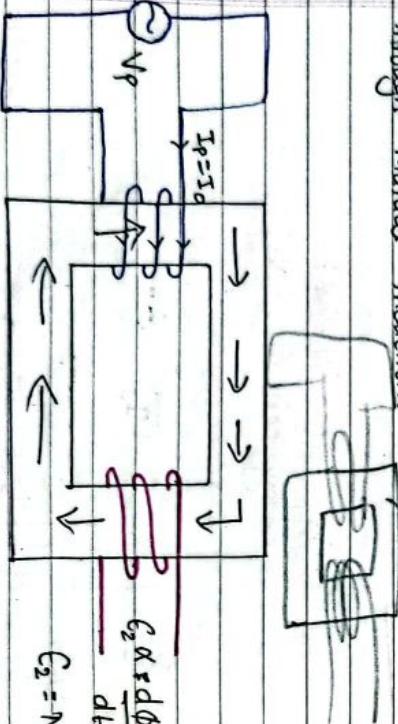The core will pass the magnetic flux (Φ) through its cross-sectional area. This flux will circulate in the ~~cross~~ core which is alternating in nature. The magnetic flux is linked with the second coil on the other limb of the core. Hence, according to Faraday's law of electromagnetic induction emf (E_2) will induced across the second coil, through mutual induction.



emf equation :

$$\ell_2 = -N_2 \cdot \frac{d\phi(t)}{dt}$$

$$\underline{E_2} = -N_2 \cdot d \underline{\Omega_m} \sin(\omega t)$$

$$f_2 = -N_2 \cdot \omega \cdot \phi_m \cos(\omega t)$$

$$E_2(\text{peak}) = N_2 w \cdot f_{\text{osc}}$$

$$E_2(\text{rms}) = E_2(\text{peak})$$

$$= \frac{\sqrt{2}}{\sqrt{2}} \cdot \psi \cdot \omega$$

$$E_{2,\text{crms}} = \frac{N_2 \cdot \phi}{\sqrt{2}}$$

$$G_{\text{2cm}} = u \cdot u_4 F \phi \cdot N_2$$

✓ Turn Ratio (a) :

$$\text{eqn ②} \div \text{eqn ①}$$

$$\frac{E_1 \text{ (rms)}}{E_2 \text{ (rms)}} = \frac{N_1}{N_2}$$

$$\frac{E_2}{E_1} = \frac{N_1}{N_2} = \text{turn ratio}$$


✓ Voltage Transformation ratio (K).

$$\text{eqn ①} \div \text{eqn ②}$$

$$\frac{E_2 \text{ (rms)}}{E_1 \text{ (rms)}} = \frac{N_2}{N_1} = K.$$

$$\therefore A = \frac{1}{K}$$

✓ Current Ratio :

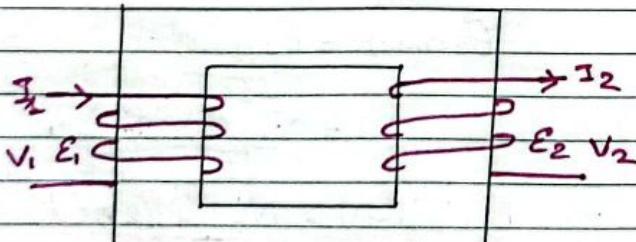

$$P_{in} = I_1 \cdot E_1 \quad P_{out} = I_2 \cdot E_2$$

(ideal transformer)

$$E_1 I_1 = E_2 I_2$$

$$\frac{E_1}{E_2} = \frac{I_2}{I_1}$$

$$\frac{E_1}{E_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$$

✓ Different types of transformer

a) Phase

→ 1Φ

→ 3-Φ

b) Core

→ Rectangular/square



→ Shell type



c) Application

→ Step up transformer

$$\boxed{N_2 > N_1}$$

→ Step down transformer

$$\boxed{N_1 > N_2}$$

$$\boxed{N_1 = N_2}$$

isolation transformer

✓ No-load operation of transformer.



(magnetize, no heat)

At no-load, transformer draw some current
To which is known as no-load primary
current.

weak form

$I_w = I \cos \theta$ (loss component)

$I_m = I \sin \theta$ (magnetic $I_m = I \sin \theta$)

$I_w = I \cos \theta = I_w$

$I_m = I \sin \theta$

vector component


I

V_P

* load operation

~~* load operation~~

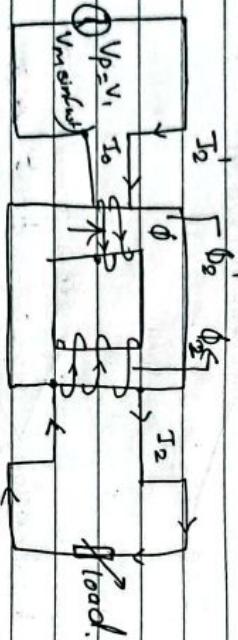at No load: $V_2 I_2 = 0$ but input is $V_i \rightarrow I_o$ (which is power less at No-load).



Φ , Φ' are equal and opposite in direction.
Hence, the net magnetic flux in the core is always remain constant at any load and is equal to Φ .

* Ideal Transformer

Ideal Transformer
Such type of transformer which has purely inductive windings without any resistance, No magnetic leakage flux and 100% efficient is known as ideal transformer.


* Practical Transformer.

Such type of transformer which has not purely inductive windings and has resistance, magnetic core leakage and not 100% efficient is known as practical / real transformer.

classmate
Date _____
Page _____


classmate
Date _____
Page _____
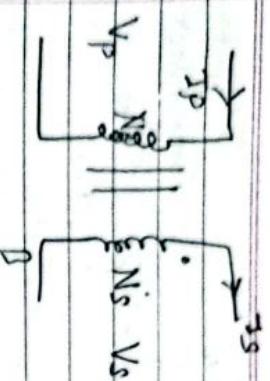
$$= \frac{P_{out}}{P_{out} + P_{losses}} \times 100\%$$



$$= \frac{P_{out}}{P_{out} + P_{coreloss} + P_{copperloss}} \times 100\%$$

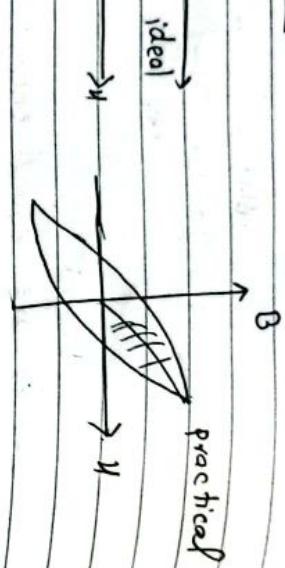Core loss = constant Copper loss = variable




$$\eta = \frac{V_s \cdot I_s}{V_s \cdot I_s + P_{core} + I_s^2 \cdot R_{req.}}$$

$$\frac{d\eta}{dI_s} = 0 \Rightarrow \text{max } \eta \text{ condition.}$$

$$V_s \cdot I_s (V_s + 0 + 2 \cdot I_s \cdot R_{req}) - (V_s \cdot I_s + P_{core} + I_s^2 \cdot R_{req})^2 = 0$$
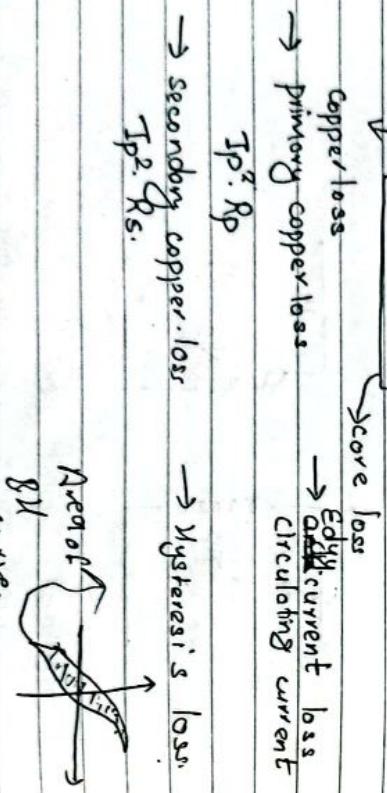
$$V_s \cdot I_s + 2 \cdot I_s^2 \cdot R_{req} - V_s \cdot I_s - I_s^2 \cdot R_{req} - P_{core} = 0.$$



$$\eta = \frac{P_{out}}{P_{in}} \times 100\%$$



$$\eta = \frac{P_{out}}{P_{in}} \times 100\%$$


$$2 I_s^2 \cdot R_{req} - I_s^2 R_{core} - P_{core} = 0.$$

$$I_s^2 R_{req} = P_{core}.$$

$$\frac{P_{out}}{P_{req}} = P_{core}$$

$$\text{Copper loss} = P_{core}$$


$$I_{max.}$$

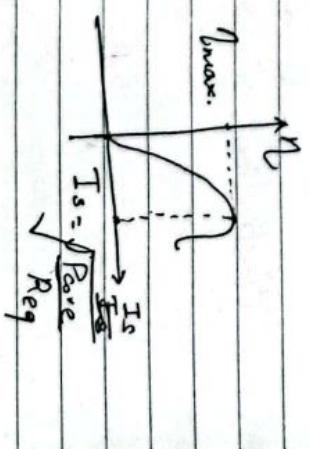

Application of Transformer

- It is used by power generation to increase the voltage level.
- It is used in transmission and distribution of power system.
- Transformers are used in audio system to increase or decrease the voltage of electricity before it is sent to speaker.
- Transformer are used in a variety of electronic devices, including computers, TV, radios or cell phones.

Induction Motor

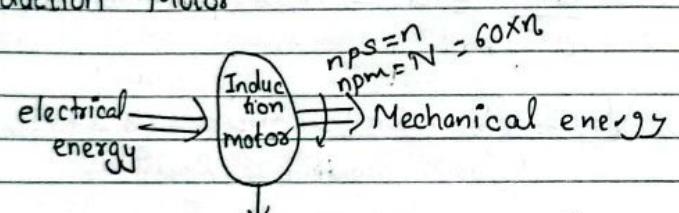

principle is based Faraday's law of electromagnetic induction.

$$E_e = P.t$$


$$P = V_{ac} \cdot I_{ac}$$

1-Φ
3Φ

$$= P_m \times t$$

$$\begin{aligned} P_m &= \text{Torque} \times \omega \\ &= T \times (2\pi n) \\ &= T \times \left(2\pi \frac{N}{60}\right) \end{aligned}$$

Construction of 3-Φ IM

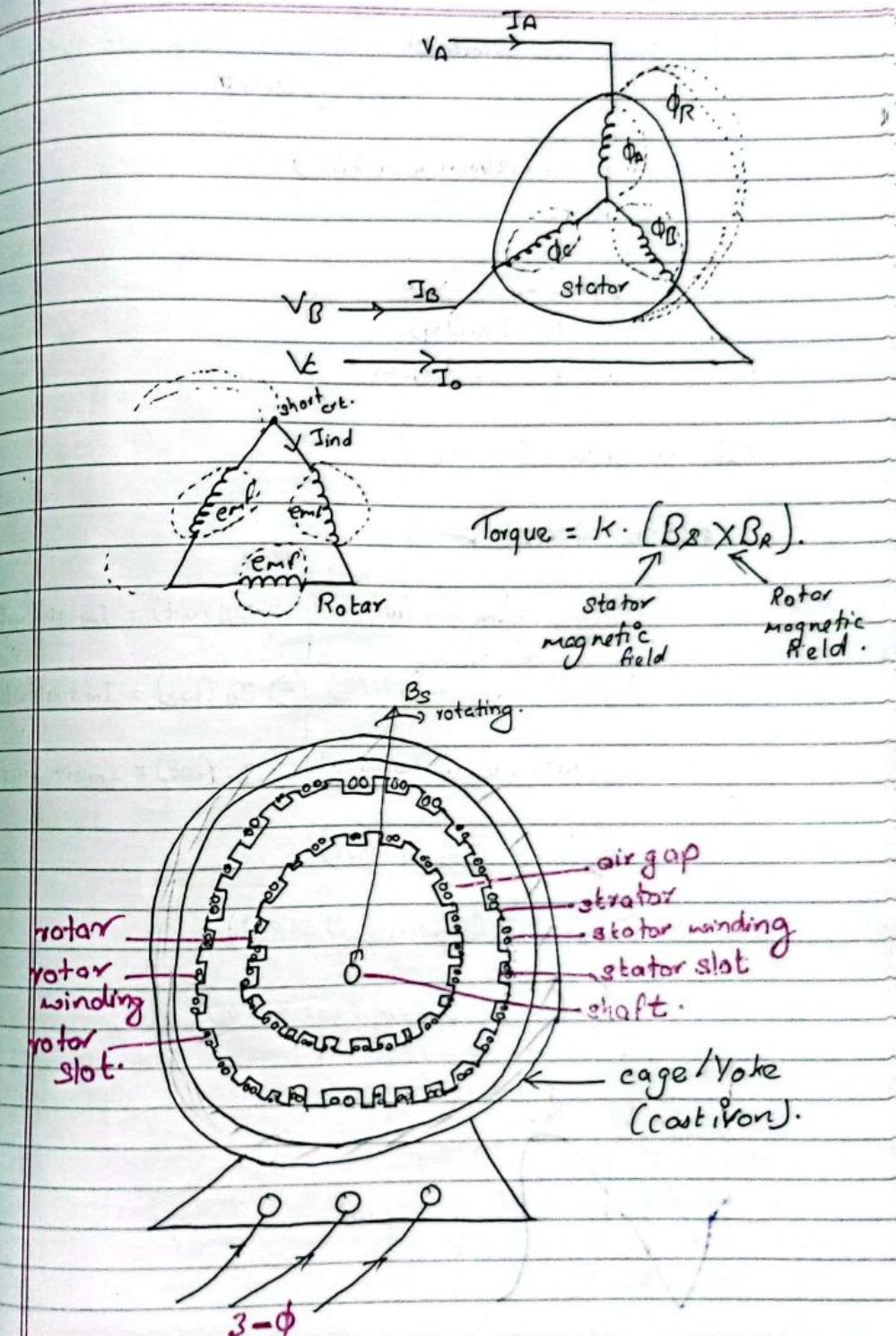

$$N_s = \frac{120f}{P} \Rightarrow \text{speed of magnetic field or synchronous speed}$$

where, f = frequency (502)
 P = pole

$$2\text{pole} = 3000 \text{ rpm.}$$

$$4 \text{ pole} = 1500 \text{ rpm.}$$

$$8 \text{ pole} = 750 \text{ rpm.}$$

Rotating Magnetic field.

Stator input 3- ϕ

$$V_A(\omega t) = V_m \sin(\omega t) \quad I_A(\omega t) = I_m \sin(\omega t)$$

$$V_B(\omega t) = V_m \sin(\omega t - 120^\circ) \quad \Rightarrow I_B(\omega t) = I_m \sin(\omega t - 120^\circ)$$

$$V_C(\omega t) = V_m \sin(\omega t + 120^\circ) \quad I_C(\omega t) = I_m \sin(\omega t + 120^\circ)$$

$$\Phi_R = \frac{2\sqrt{3}}{2} \Phi_m \cos 30^\circ$$

$$= 2 \cdot \frac{\sqrt{3}}{2} \Phi_m \times \frac{\sqrt{3}}{2}$$

$$\Phi_R = 1.5 \Phi_m$$

$$\text{at } \omega t = 120$$



$$\Phi_R = \frac{\sqrt{3}}{2} \Phi_m \cdot \cos 30^\circ$$

$$\Phi_B = 2.0A$$


$$\Phi_R = \Phi_B = 2 \cdot \frac{\sqrt{3}}{2} \Phi_m \cdot \cos 30^\circ$$

$$\Phi_R = 1.5 \Phi_m$$

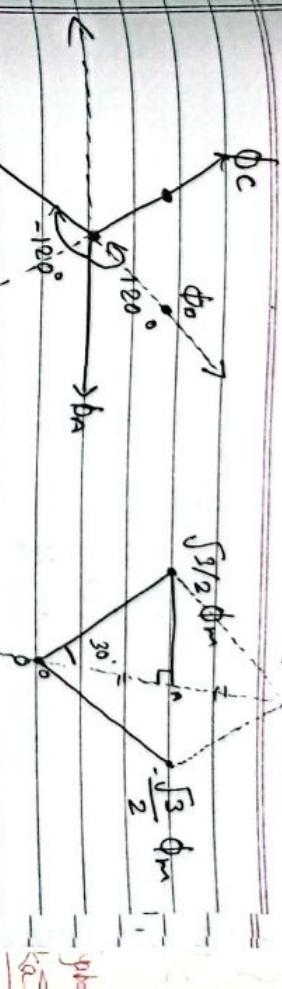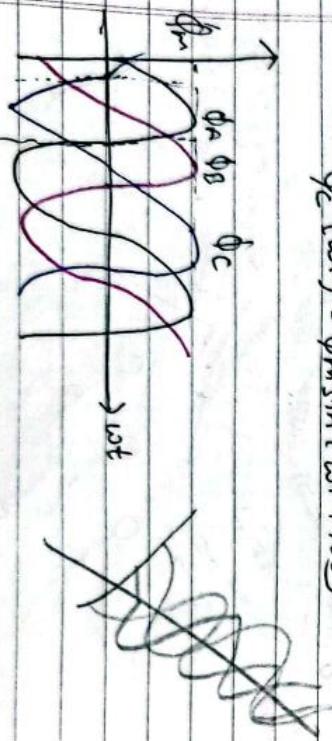Similarly for every ωt : $\Phi_R = 1.5 \Phi_m$.



Mr. Naresh

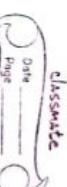


MR = Variable (because it depends on load).

Stator frequency.

$$f = \frac{N_s \cdot P}{120}$$

Rotor frequency
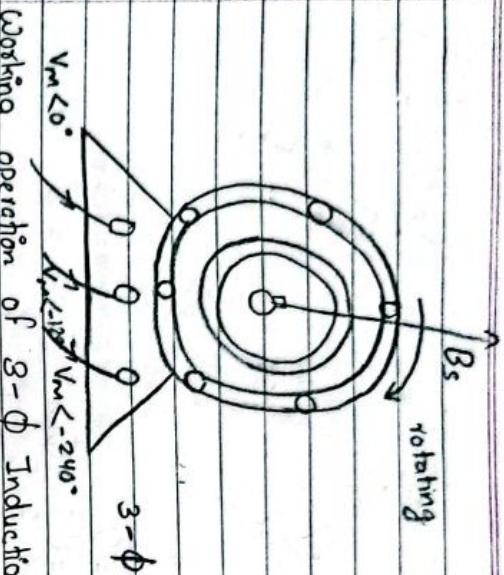
$$f_r = \frac{(N_s - N_r) \cdot P}{120} \quad \text{②}$$




Working operation of 3-Φ Induction Motor.

- When we supply 3-Φ input to the stator there is production of rotating magnetic field which cuts the rotor winding and voltage induced in the rotor winding.
- Due to the fact that rotor windings are short circuited, current will flow in the rotor winding.
- The rotor current produced another magnetic field.
- The torque is produced as a result of the interaction of these two magnetic fields i.e.

$$T_{ind} = K \cdot (B_s \times B_r)$$

$$\text{Slip speed} = N_s - N_r$$

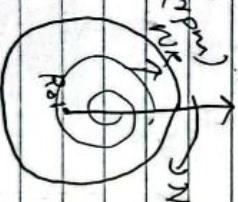

$$N_s = \frac{120f}{P}$$

$$f_r = \frac{f}{s}$$

stator
rotor
 $s = \frac{N_s - N_r}{N_s}$

eqn ② ÷ eqn ①

$$\frac{f_r}{f} = \left(\frac{N_s - N_r}{N_s} \right) = s$$

Ques: What will be the speed of rotor if the pole of stator is 6 and frequency 50Hz and rotor frequency is 120 cycle per minute.

$$\text{Soln: } f_r = 120 \text{ cycle/min}$$

$$= 120/60$$

$$\text{Slip (\%)} = \frac{N_s - N_r}{N_s} \times 100\%$$

$$\therefore \alpha = \frac{f_r}{f} = \frac{2}{50} = 0.04$$

$$N_s = \frac{120 \times 50}{6}$$

$= 1000 \text{ rpm.}$

$$S = N_s - N_R$$

$N_s.$


$$0.04 = \frac{1000 - N_R}{1000}$$

$$40 = 1000 - N_R$$

$$\therefore N_R = 960 \text{ rpm}$$

* Rotor

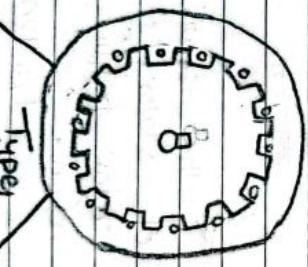Rotor is a hollow laminated core having slots and copper winding which is mounted on the shaft.




Squirrel cage

Wound rotor or

(In this copper or aluminum slipping rotor bar are placed on the (In this rotor similar to the rotor slot).



Type

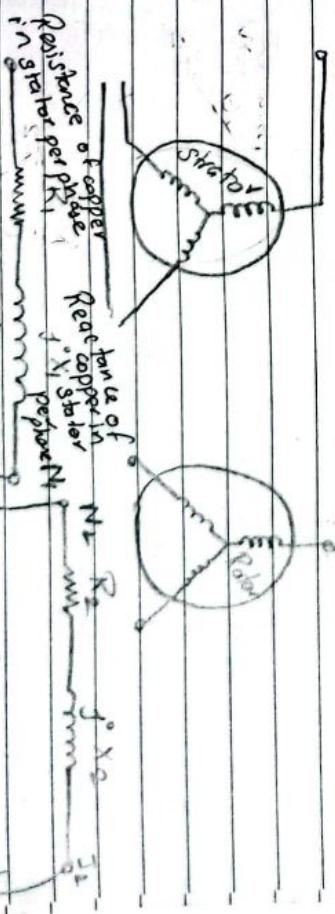

* Equivalent Circuit Model of 3-Φ IM.

- It is economical & simpler. It is costly.
- It is rugged, so requires less maintenance.
- Torque cannot be controlled by using external torque.
- Speed cannot be controlled by using external resistance.

Squirrel cage

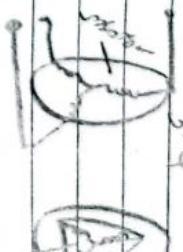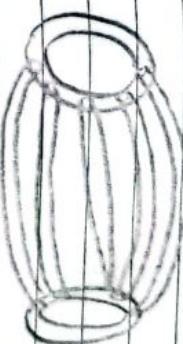


rotor

b/w

3-Φ

phase

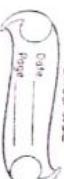

Date _____


Page _____

classmate

Date _____

Page _____

Equivalent circuit Model of T.M

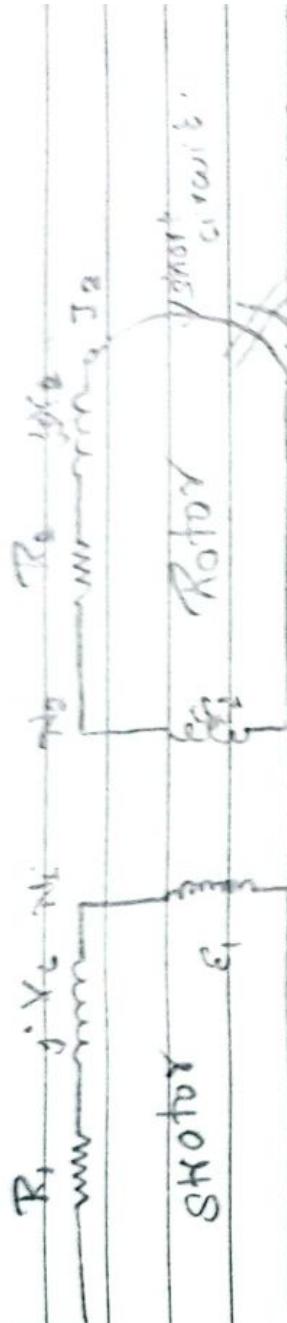

Case 1 Rotor Rotating ($N_R \neq 0$)

$$\delta = \frac{N_s \cdot N_R}{N_s + N_R}$$

i) Voltage Equation :

$$\delta E_2 = \frac{N_2}{N_1} \cdot E_1$$

ii) Current equation :

$$I_2 = \frac{\delta \cdot E_2}{R_2 + j(sX_2)}, |I| = \frac{\delta \cdot E_2}{\sqrt{R_2^2 + (sX_2)^2}}$$

$$p.f = \cos \theta = \frac{R_2}{\sqrt{R_2^2 + (sX_2)^2}}$$

iii) Torque $T = k(B_s \times B_r)$



$$= k \cdot E_2 \cdot \frac{\delta \cdot E_2}{\sqrt{R_2^2 + (sX_2)^2}} \times \frac{R_2}{\sqrt{R_2^2 + (sX_2)^2}}$$

$$\boxed{T = \frac{k \cdot \delta \cdot E_2^2 \cdot R_2}{(rotating) R_2^2 + (sX_2)^2}}$$

Condition for maximum torque

$$\frac{dT}{d\delta} = 0$$

$$K \cdot \delta \cdot C_2^2 \cdot R_2 \left(0 + 2\delta X_2^2 \right) - \left(R_2^2 + \delta^2 X_2^2 \right) K \cdot C_2^2 \cdot R_2 = 0$$

$$(R_2^2 + (\delta X_2)^2)^2$$

$$\text{or, } \delta (2\delta X_2^2) - (R_2^2 + \delta^2 X_2^2) = 0$$

$$\text{or, } 2\delta^2 X_2^2 - R_2^2 - \delta^2 X_2^2 = 0$$

$$\text{or, } \delta^2 X_2^2 - R_2^2 = 0$$

$$\text{or, } \delta^2 = \frac{R_2^2}{X_2^2}$$

$$\therefore \delta = \frac{R_2}{X_2} \quad X_2 > R_2 \quad \{ \text{So, the value of } \rho \text{ is less than 1.} \}$$

$$\text{Rotating } = \frac{K \cdot \delta \cdot C_2^2 \cdot R_2}{R_2^2 + \delta^2 + X_2^2}$$



$$\text{if } R_2^2 \ggg (S X_2)^2 \quad \text{if } R_2^2 \lll (S X_2)^2$$

$$T_R = K \cdot \delta \cdot C_2^2 \cdot R_2 \quad , \quad T_R = \frac{K \cdot \delta \cdot C_2^2 \cdot R_2}{\delta^2 X_2^2}$$


$$\therefore T_R \propto S \quad \therefore T_R \propto \frac{1}{S}$$

Torque (linear region)

Working region.


Fig: Torque-Slip

X-tics

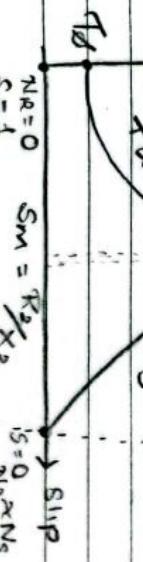

✓ losses and efficiency.

Date _____
Page _____

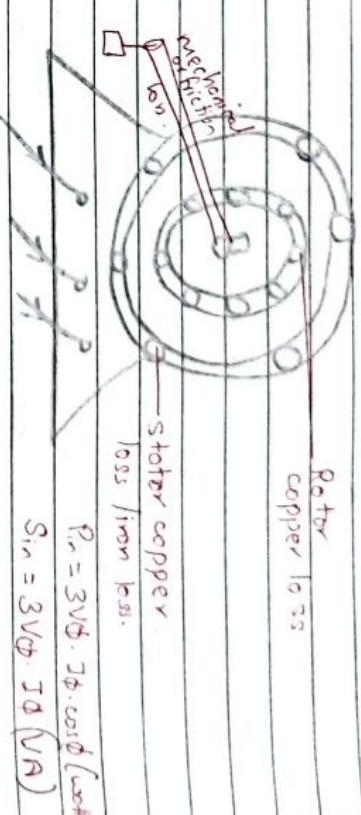

P_{in}	Stator (motor)	P_{in}	Rotor	P_{in}	Mechanical Power	P_{mech}
1000 or 10000	= Stator = Rotor	P_{in} - copper	= Rotor	P_{in} - shaft	= shaft - friction	= Power

Efficiency = $\eta_{motor} = \frac{P_{in} (motor)}{P_{in} (stator)} \times 100\%$

$$\eta_{motor} = \frac{P_{in} (motor)}{P_{in} (stator)} \times 100\%$$

$$\eta_{motor} = \frac{P_{in} (motor)}{P_{in} (stator)} \times 100\%$$


Applications of 3-Φ IM:

- Electric train engine
- Used as cooling fan.
- Printing machines
- Rolling mills
- In water pump motor

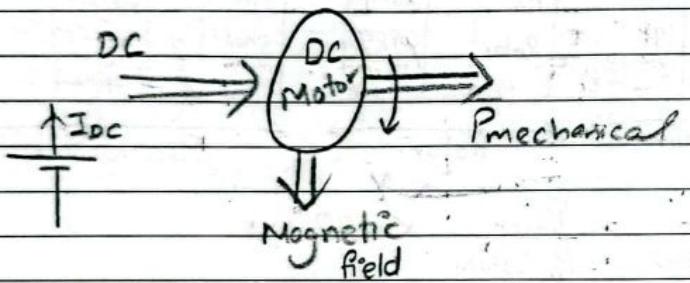- vi) In hydraulic for pumping the fluid.
 vii) Drilling machine.
 viii) Motor or refrigerator /washing machine
 ix) Cooler motor
 x) Industrial Drives
 xi) Agricultural and industrial pump

Q-3 DC Motor:


It is an electro-mechanical devices which converts DC electrical power to mechanical power.



DC Motor Principle :


It's action is based on the principle that when a current carrying conductor is placed in a magnetic field, it experiences a mechanical force whose direction is given by Fleming's left hand rule and whose magnitude is given by

$$F = B I L \sin \theta$$

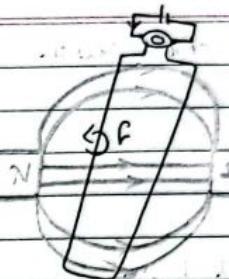

$$\begin{aligned} \theta &= 0^\circ \\ f_{\min} &= 0 \\ \theta &= 90^\circ \\ f_{\max} &= BIL \end{aligned}$$

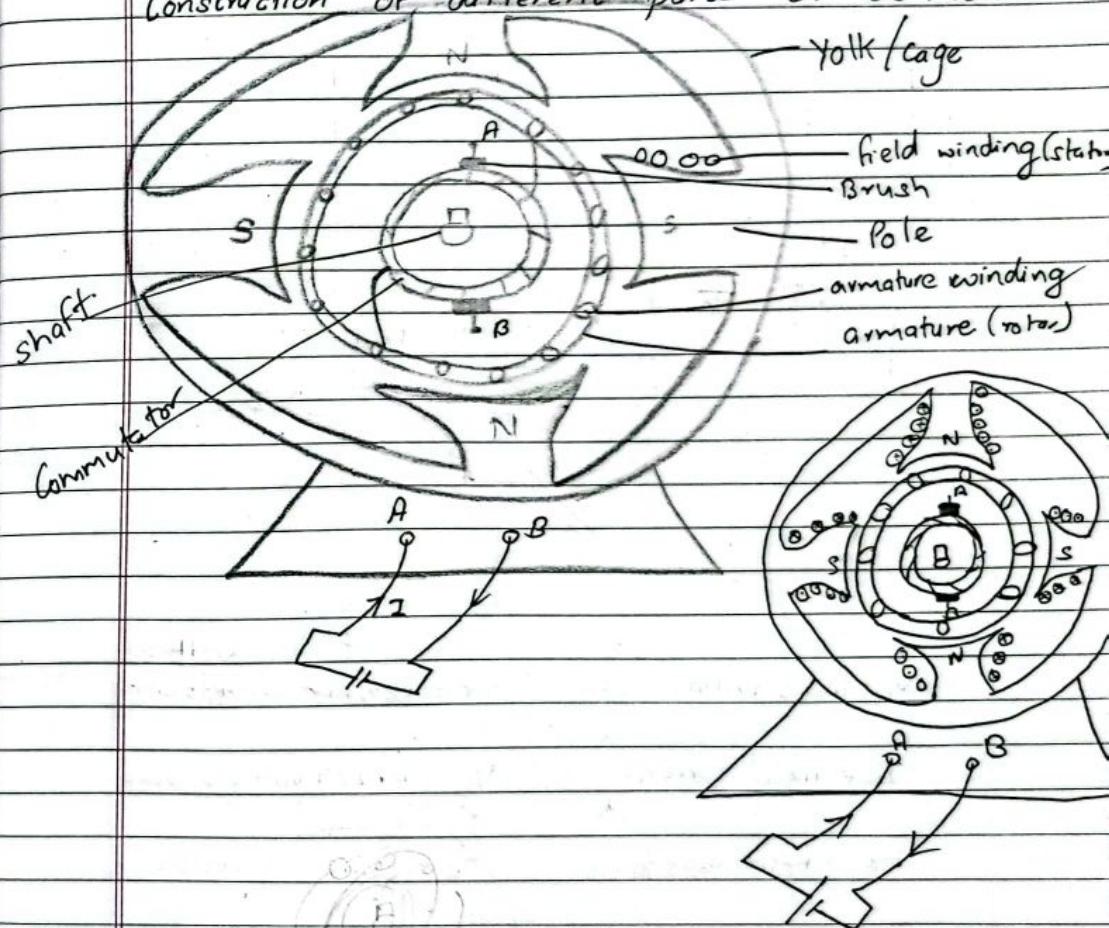Construction of different parts of DC Motor.



Equivalent circuit Model of DC Motor.



Back emf or armature Voltage (E_a, E_b)

When the armature of a DC motor rotates under the influence of the driving torque, the armature conductors move through the magnetic field and hence emf is induced in them as in a generator. The induced emf acts in opposite direction to the applied voltage V_t and is known as back emf i.e. E_b .

$$E_b = \frac{d\phi}{dt} \quad \text{where, } d\phi = \frac{\text{pole flux}}{60/N}$$

$$dt = \frac{60/N}{\text{rpm}}$$

$$\begin{aligned} E_b &= P \cdot \phi \\ &= \frac{60/N}{P \cdot \phi \cdot N} \end{aligned}$$

where,

$$\begin{aligned} P &= \text{Pole} \\ \phi &= \text{flux} \end{aligned}$$

N = no. of revolution per min (rpm).

If there are Z no. of conductor

$$E_a = \frac{P \cdot \phi \cdot N}{60} \times Z$$


~~loop winding~~ $E_a = \frac{P \cdot \phi \cdot N}{60} \times \frac{Z}{P}$

~~wave winding~~ $E_a = \frac{P \cdot \phi \cdot N}{60} \times \frac{Z}{2}$

V_t = field voltage
 ∇_t = terminal voltage


I_F = field current
 V_b = brush voltage drop
 R_F = field resistance
 R_a = armature resistance

$(E_a, E_b = \text{Back emf})$

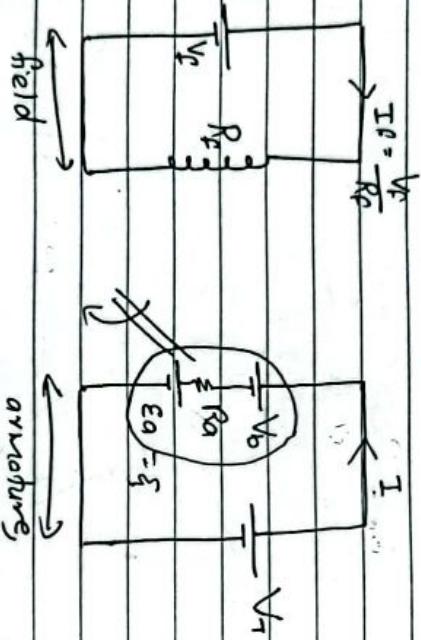

Different type of DC Motor.

a. Separately Excited DC Motor.

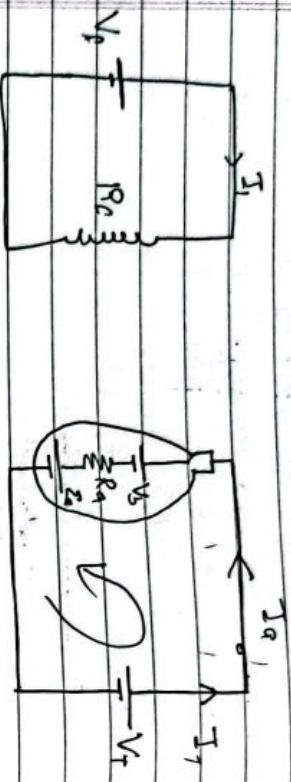


$$V_f = I_f R_f \quad I_t = I_a \text{ (KCL)}$$

$$I_f = \frac{V_f}{R_f} \quad V_t = V_b + I_a R_a + E_a$$

brush armature
copper or back
voltage drop

b. Self Excited DC Motor.

i.) Shunt type DC motor.

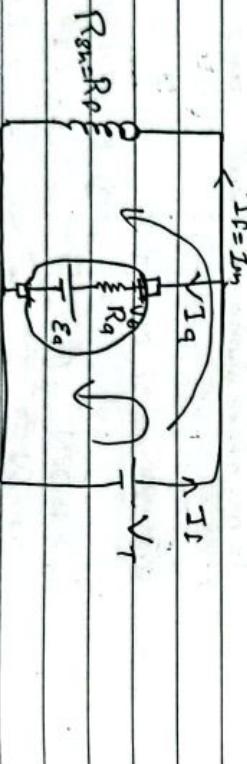

$$I_f = I_m \quad R_{sh} = R_f$$


$$I_a = I_{se}$$

$$V_t = I_{se} R_{se} + V_b + I_a R_a + E_a$$

$$V_t = V_b + I_a R_a + E_a$$

ii) Series DC Motor


$$R_f = R_{se}$$

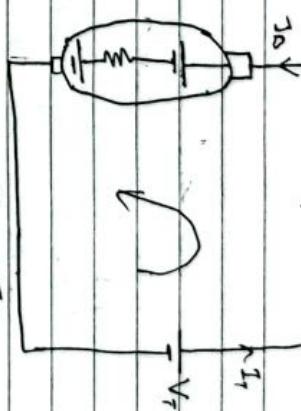

$$V_t = I_{se} \cdot R_{se} + V_b + I_a R_a + E_a$$

iii) Compound type DC motor.

1) long shunt : short shunt

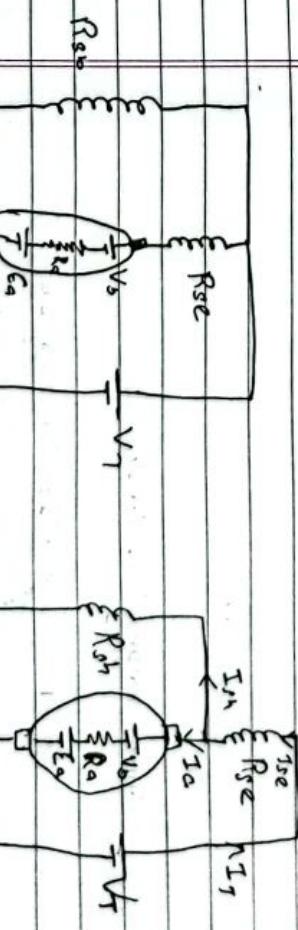

$$I_t = I_{se} + I_{sh}$$

$$I_a = I_{se}$$

$$I_{se} = I_a + I_{sh}$$

$$V_t = I_{se} R_{se} + V_b + I_a R_a + E_a$$


$$V_t = I_{se} R_{se} + V_b + I_a R_a + E_a$$

$$V_t = I_{sh} \cdot R_{sh}$$

X Torque of DC Motor

Torque is produced around the circumference of rotor starts rotating in the conductors which lie near the surface of the rotor at a common radius from its centre.

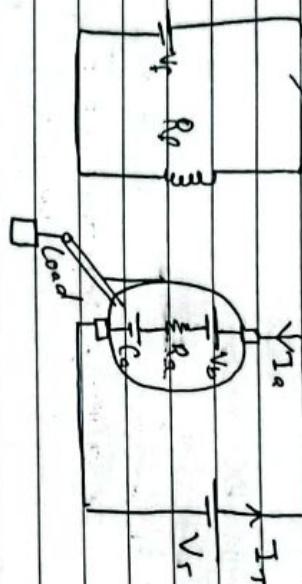In motor torque is transferred to the shaft of the rotor and drives the material load.



$$T = \frac{\Phi \cdot P}{2\pi} \left(\frac{Z}{A} \right) \times I_a$$

$$T \propto \Phi \cdot I_a$$

Torque is directly proportional to Φ of armature current.

21 March.
Losses and efficiency of DC Motor.

$$V_r \cdot I_s = I_r \cdot V_b + I_a^2 \cdot R_a + I_a \cdot G_a$$

$V_r \cdot I_s$ = power in armature
 $I_r \cdot V_b$ = power in iron
 $I_a^2 \cdot R_a$ = copper loss
 $I_a \cdot G_a$ = friction loss.

(sparking).

if there is no mechanical loss.

$$P_m = T \cdot \omega \quad \dots \quad (1)$$

$$P_{mechanical} = T_a \cdot \omega_0$$


$$\tau \omega = I_a \cdot G_a$$

$$T = \frac{I_a}{\omega} \times G_a$$

$$G_a = \frac{\Phi \cdot P \cdot N}{60} \left(\frac{Z}{A} \right)^2 P$$

(load) (top)
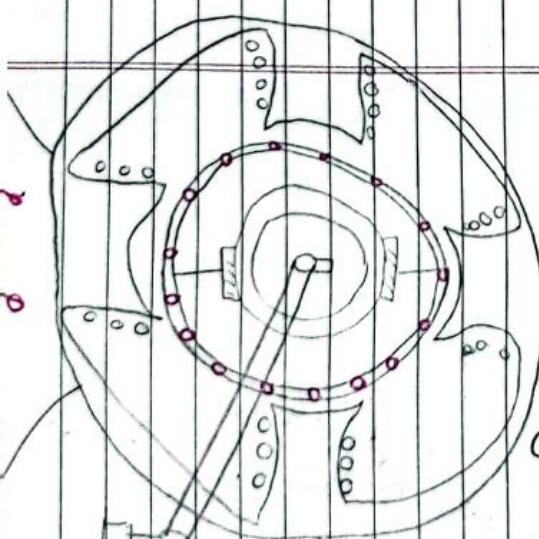
$$T = \frac{\Phi \cdot P}{60} \left(\frac{Z}{A} \right) \times \frac{I_a}{2\pi N / 60}$$



Avg equivalent Circuit Model
of long shunt com pos

There are three different types of losses

i) Copper loss

\rightarrow Armature copper loss ($I_a^2 \cdot R_a$)

\rightarrow Series copper loss ($I_{se}^2 \cdot R_{se}$)

\rightarrow Shunt copper loss ($I_{sh}^2 \cdot R_{sh}$)

ii) Magnetic loss / Iron loss / core loss / constant loss

\rightarrow Hysteresis loss

\rightarrow Eddy current loss.

iii) Mechanical loss

\rightarrow frictional loss.

\rightarrow Windage loss.

$$\eta = \frac{P_{mechanical}}{P_{input}} \times 100\%$$

If there is no friction loss.

$$P_{mech} = P_a = C_a \cdot I_a$$

iii) Compound DC Motor.

\rightarrow They are used rarely in industry but if used they provide constant speed and high torque.

e.g.: Presses, shears, etc.

* Synchronous Generator

In industry and generation houses uses 99% of the Mega-watt synchronous generator as a turbine. It provides frequency regulation and voltage regulation. Synchronous generators are used as voltage control in power stations.

Synchronous generator have mainly three parts i.e.


a) Stator: It contains various part which include

Applications of DC Motor

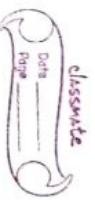i) shunt DC Motor

\rightarrow where we need constant speed at no-load or full motor.

e.g.: Lathes, drills, boring mills, spinning machines.



There are three different types of losses.

i) Copper loss

- Armature copper loss ($I_a^2 \cdot R_a$)
- Series copper loss ($I_s^2 \cdot R_{se}$)
- Shunt copper loss ($I_{sh}^2 \cdot R_{sh}$)

ii) Magnetic loss / Iron loss (core loss / constant loss)

- Hysteresis loss
- Eddy current loss.

iii) Mechanical loss

- frictional loss.
- Windage loss.

$$\eta = \frac{P_{mechanical}}{P_{input}} \times 100\%$$

If there is no friction loss.

$$P_{mech} = P_a = E_a \cdot I_a$$

$$\eta = \frac{P_a}{P_{in}} \times 100\%$$

$$= \frac{P_a}{P_{at \text{ Presses}}} \times 100\%$$

Applications of DC Motor

i) Shunt DC Motor

→ where we need constant speed at no-load or full motor.

e.g.: Lathes, drills, boring mills, spinning machines.

ii) Series DC Motor

→ where we need variable speed i.e. speed is low and torque is high at starting and high speed and low torque.

e.g.: Electric traction train, cranes, elevators, air compressor, vacuum cleaner.

iii) Compound DC Motor.

→ They are used rarely in industry but if used they provide constant speed and high torque.

e.g.: Presses, shears, etc.

* Synchronous Generator

In industry and generation houses uses 99% of the Mega-watt synchronous generator as a turbine. It provides frequency regulation and voltage regulation. Synchronous generators are used as voltage control in power stations.

Synchronous generator have mainly three parts i.e.

a) Stator: It contains various part which incl

armature resistance, leakage reactance, armature electrical.



$$E_a = I_a R_a + I_a j X_a + V_r$$


March. 23

Synchronous Generator


Working principle and emf equation.

T_F works on the principle of electromagnetic induction like DC generator. In synchronous generator, the field poles are rotating and armature conductor (stator conductors) are stationary but in ~~both~~ DC generator, the field poles are stationary and armature conductors are rotating.

Field.
Armature conductor.

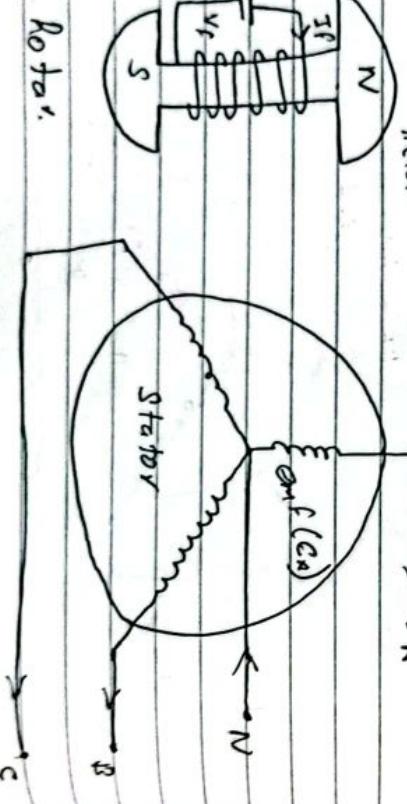

Circuit diagram per phase.

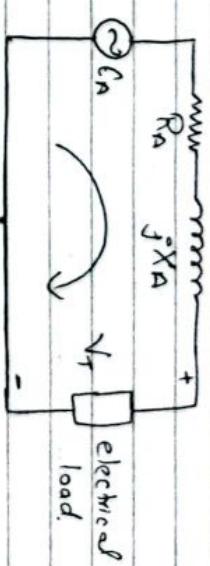

$E_a = I_a R_a + j I_a X_a + V_r$

average value of emf (E_a) = $\frac{d\phi}{dt}$

$d\phi = P \cdot \dot{\phi}$

$dt = \frac{1}{n - 1} \text{ rps}$

$= \frac{1}{N/60} \text{ rpm}$

$$E_a = \frac{\Phi \cdot P}{60 / N}$$

$$E_a = \frac{\Phi \cdot P N}{60}$$

$$E_a = \frac{\Phi \cdot P}{60} \times \frac{120 f}{P}$$

$E_a = 2 \Phi \cdot f \cdot (\text{Avg. Value per conductor})$

If there are Z no. of conductor

$$E_A = 2 \cdot \phi \cdot f \cdot Z$$

where,

$$Z = 2 \cdot \pi \quad [f = \text{No. of turn of conductor.}]$$


$$E_A = 4 \cdot \phi \cdot f \cdot \tau$$

RMS value of S.C. $E_{\text{rms}} = 4.44 \cdot \phi \cdot f \cdot \tau$

$$E_{\text{rms}} = 4.44 \cdot \phi \cdot f \cdot \tau$$

Application of Synchronous Generator

- Synchronous machines are used in modern societies like industry, commercial, agriculture and domestic sectors.
- They usually operate together, forming a large power system supplying electrical energy to the load or consumers.
- They are built in large units their rating ranging from 10 to 1000 megawatts.
- Smaller synchronous machines are sometimes used for (private generation) and also steadily by units, with diesel engines or gas turbines as prime mover.

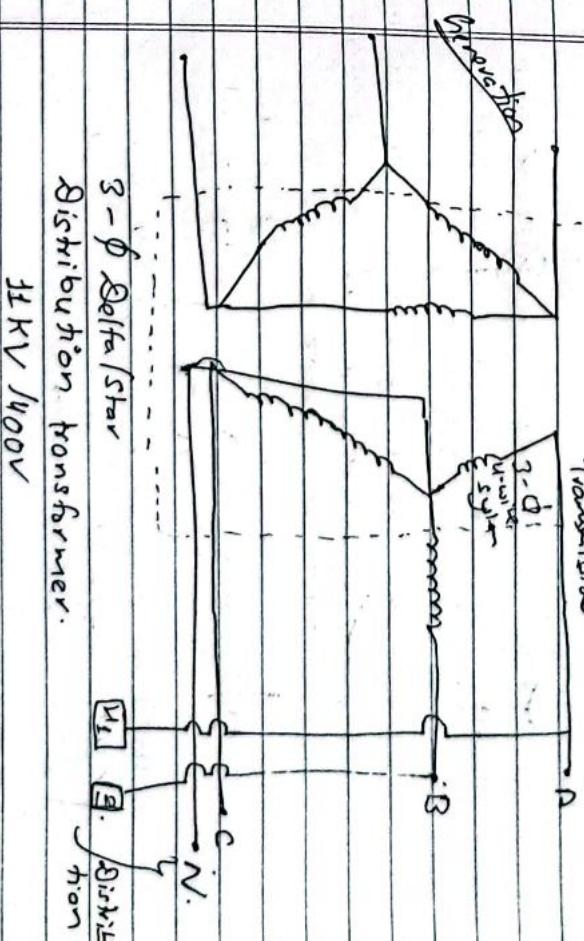

CHAPTER - II

Electrical Installation (10 mark).

Components of Power supply system.

→ Generation (By which electricity is carried from one place to another place)

→ Distribution (to the consumers provided by the electricity authority).

Transmission

Generation

3-phi
unit

impose

B

C

N.

3-phi Delta/Star

Distribution transformer

11 KV / 400 V

Large unit of 10 to 100 megawatt.

Small SC are used in private generation.

Large power system supply plants.

Used in medium size being like industry, commerce, agriculture etc.


Electrical wiring Components:

Electrical wiring is generally refers to insulated conductor used to carry current and associated device. Domestic electric appliances

like lights, etc., fans, washing machines, water pumps etc. are connected to the supply through insulated wire which are controlled by switch ... The wiring diagram gives the connections of different appliances to the supply within a house or building.

→ Different types of wiring method :

a) Series connection.

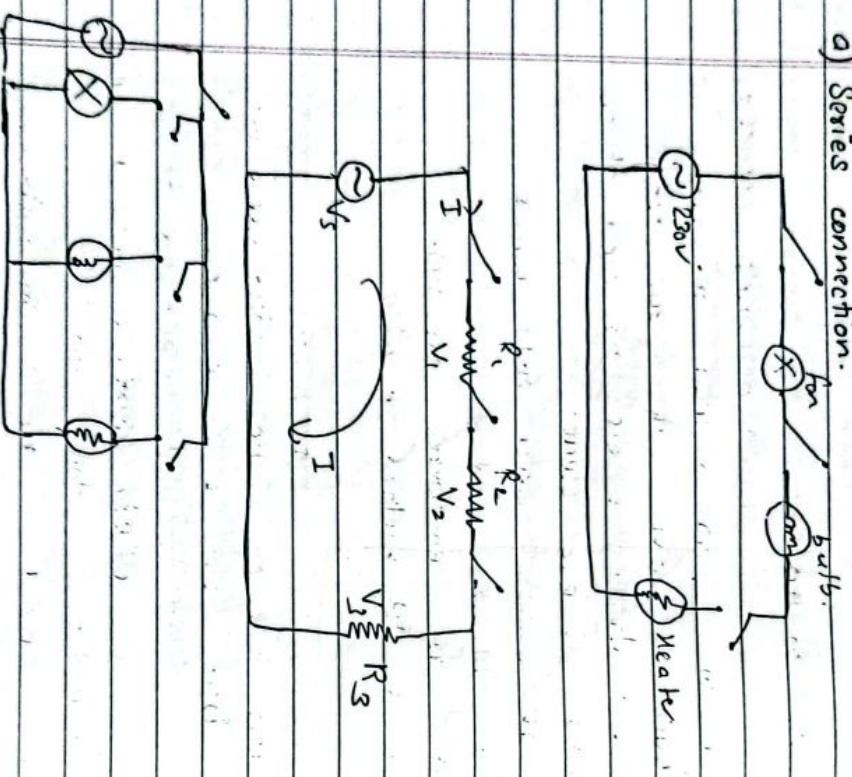

Types of wiring based on material used.

i) Cleat wiring

In this type of wiring, wood or plastic cleats are fixed to walls or ceilings at regular intervals i.e. 0.6m between each other.

- PVC insulated cables are taken through the holes of each cleat.
- Cleat support and hold wires
- This is less costly.
- Used for temporary installation.
- It is old method of wiring.

ii) CTS wiring or TRS wiring.

- This type of wiring is also used for house wiring and is quite cheap.
- Cab tyre sheathed (CTS) wire or Tough rubbe sheathed (TRS) wire is normally used as conductor for this wiring.
- This wires are run on the teak wooden battens which are fixed on the wall or ceiling by means of screws and wooden plugs.

Types of wiring based on consumers.

i) Domestic wiring

ii) Commercial wiring

iii) Industrial wiring.

iii) Batten wiring

- In this, insulated wires are run through the straight teak wooden battens.
- The wooden battens are fixed on the ceiling or walls by plugs and screws.
- This system takes less time to install.
- These are mainly used for indoor installation.

iv) Conduit wiring


- In this wiring, PVC cables are taken through either PVC conduit pipes or through steel conduit pipes.
- This conduit wiring can be either surface conduit wiring or concealed conduit wiring.
- If the conduits are run inside the surface of the walls or ceilings, they should be covered with plastering, it is called concealed wiring.
- Surface conduit wiring is used in industry to connect heavy motors or load.

- Concealed wiring is the most popular in residential buildings.


- This method is the safest method of wiring and also looks clean and neat.

Electrical Wiring Representation

a) Block Diagram

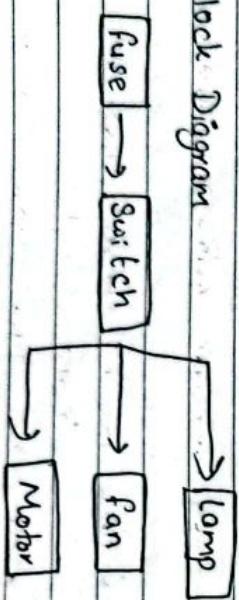

c) Circuit Diagram

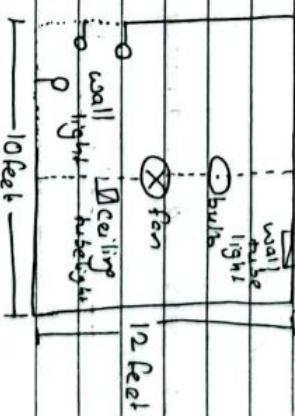

v) Wiring Accessories

- i) Switch
- ii) Socket
- iii) Lamp holder
- iv) Plugs
- v) fuse
- vi) MCB / MCCB
- vii) Distribution Boards
- viii) Wires and Cables.
- ix) PVC Pipes
- x) Led Bulbs / Tubelight.

w) Protective Devices, their constructions and sizing.

- i) Fuse: A fuse is a device used to protect the circuits and equipments against overloads and short circuits.

b) Line Diagram



- fuse element materials have low melting point and high conductivity.
- Fuse operation is based on the heating effect of the current when flow through element.
- Its rating can start from few mA to several kA (kilampere).
- different types of fuse are used in application nowadays.
 - i.e. - Rewireable fuse
 - Cartridge fuse.
 - High Rupturing capacity fuse.

Symbol of fuse are



Safety Devices.

a. **Fuse**

b. **MCB**

MCB stands for Miniature Circuit Breaker. It is an electromechanical devices which can turn a circuit ON and OFF whenever there is a fault in the circuit, it automatically operates to turn off the circuit. Generally MCB provides short-circuit protection to a circuit. It senses the overcurrent in the circuit caused by short circuit and trips the circuit.


An MCB consists of two contacts, one is moving contact and the other is fixed contact when the circuit current becomes abnormally high, the movable contact separated from fixed contact to make the circuit open and disconnect it from the supply mains. The MCB come in various poles like single-pole, double pole and 3-pole.

$\rightarrow 1.25$ for class P

$\rightarrow 1.25$ and 1.5 for class Q

$\rightarrow 1.5$ and 2.5 for class R

e.g.

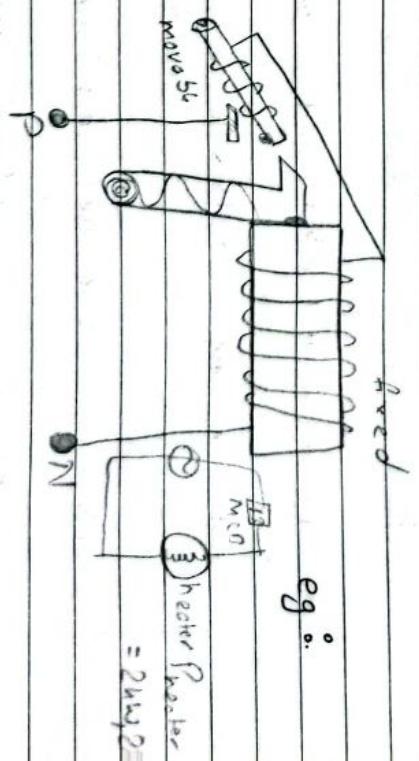

Eg : What is the minimum rated current of the 20A P class fuse that will be operated?

$$1.25 = \frac{\text{Rated min fusing factor}}{20 \text{ A}}$$

$$\text{Rated min fusing factor} = 25\text{A}$$

- MCB rated current not more than 100A.

- MCB of different current rating are available

i.e. 6, 10, 13, 16, 20, 25, 40, 50, 63, 80 and 100A



c) MCCB

MCCB stands for Molded Case Circuit Breaker. MCCBs are the protecting devices having trip circuit thermal or thermomagnetic or electronic type. The MCCBs provide protection against overcurrent due to short circuit, earth fault, under voltage, etc.


It is used to protect the loads over 100A and motor protection circuit. It also available in single pole, double-pole and triple pole versions. (also on 4-pole).

→ Differences between MCB and MCCB.

MCB	MCCB
- Type of switch which protects the system from overloaded current.	Protects the equipments from over temperature and fault current.
- Miniature Circuit Breaker	Molded Case Circuit Breaker
- Available in single, two and 3-pole version.	Available in single, two, three and four pole version.
- Current rating up to 100A	Current rating from 10-20A up to 100A
- Cannot be control remotely	- Can be control remotely.
- Used for domestic purpose like house wiring.	Used commercially and in industries.

→ Wires and cables.

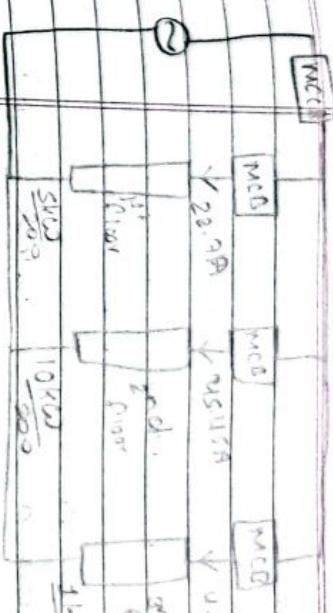Conductors : A conductor has many free electrons so is good at transferring electrical current e.g. Copper - high conductivity
- easily obtained
- heavier or more expensive than aluminum
- Copper wire is used in house wiring.



Aluminum : It has 60% conductivity than copper.

- Cheap and lighter than copper
- Used for small loads which takes less amount of current.

Using these ~~wires~~ conductors and PVC insulators wires and cables are made.

Wires :

- Domestic or small industry wiring

Cables :

- small and big industries.

- distribution lines.

- Transmission lines.

Different types of wires:

Six types of wires:

- Vulcanised Indian rubber wire (V.I.R)
- Tough rubber sheathed wire (T.R.S)
- Poly Vinyl chloride Wire (P.V.C.)
- lead alloy sheathed wire.
- weather proof wires.
- flexible wires.

Different types of cables:

The type of cables basically decided based on the voltage level for which it is manufactured and material used for the insulation such as paper, cotton, rubber, etc. The classification of cables according to the voltage level is,

- Low Tension Cables (L.T cables)


- Medium or High Tension Cables (H.T cables).

Determination of a size of a cable or wire:

The current carrying capacity of any conductor depends directly on its length and inversely on its cross-sectional area. i.e.

$$R \propto \frac{l}{A}$$


$$R = \rho \frac{l}{A}$$

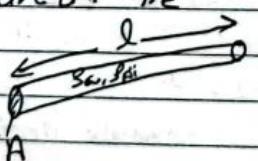

According to IEC standard at any point below power supply terminal and installation of load voltage drop should not increase about 2.5% of the supply voltage.

Moreover for given load except the known current, there should be 20% extra scope of current for additional load for future emergency needs.

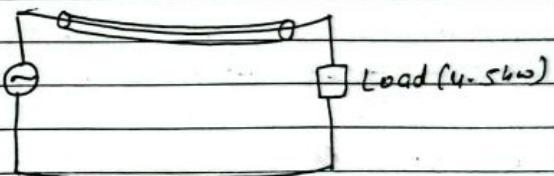e.g.: for electrical wiring installation in a building, Total load is 4.5kW and supply voltage is 220V. find the most suitable size of cable for energy meter to subcircuit.



$$P_T = 4.5 \times 10^3 \text{ watt.}$$

$$20\% \text{ of } P_T = \frac{20}{100} \times 4500 = 900 \text{ watt.}$$

$$P_{\text{Total}} = 4500 + 900 = 5400 \text{ watt.}$$

$$P_T = V_T \cdot I_T = 5400$$

$$I_T = \frac{5400}{220} = 25.54 \text{ A.}$$

for 25.54A copper size size should be 4.5 mm². ~~size~~ (Table).

Eg:- Determine the size of a copper cable for MCB to SDB require to carry the maximum current of 60A. It is given that length of cable are 200m and 100m, the permissible voltage drop is 2% of the supply voltage. The supply system is single phase whose voltage is 220V. Rating of copper is given below.

area of conductor (mm^2)	1.5	2.5	4	6	10	15	25	50
current reading.	21	22	36	45	60	72	99	104
MCB	90	95	120	150				
SDB	115	195	240	246				

$$S = 1.68 \times 10^{-8}$$

$$I = \frac{S \cdot l}{R} = 4.44$$

$$R = \frac{10.17 \times 1.68 \times 10^{-8} \times 300}{4.44}$$

$$R = 11.64 \text{ mm}^2$$

Earthling for electrical Equipment and Appliances.


Equipment earthing is a connection done through a metal link between the body of any electrical appliances, or neutral point, or the case may be, to the deeper ground soil. The metal link is normally of MS plate, or I wire which should be penetrated to the ground earth grid.

$$V_d = \text{Twire} \times R_{\text{wire}}$$

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

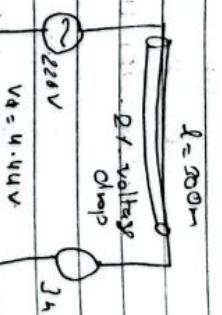


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

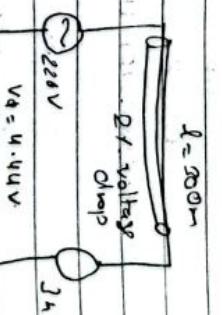


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

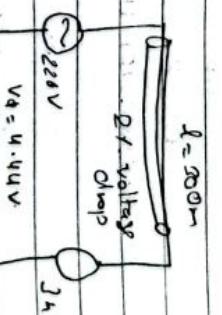


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

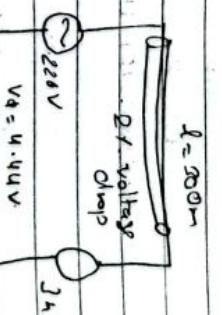


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

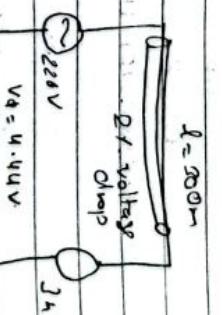


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

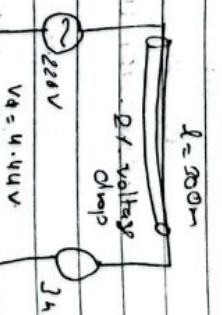


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

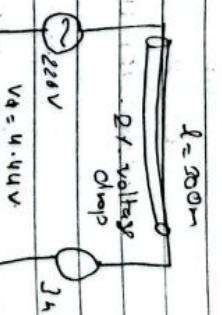


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

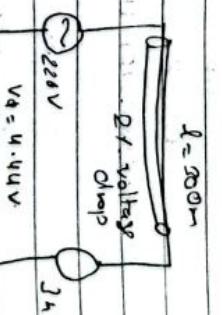


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

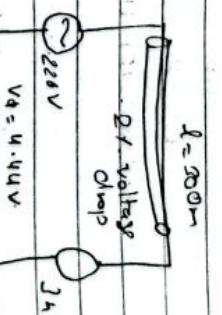


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

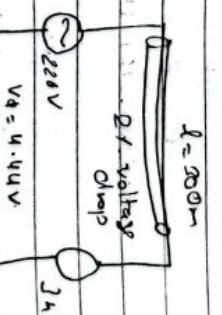


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

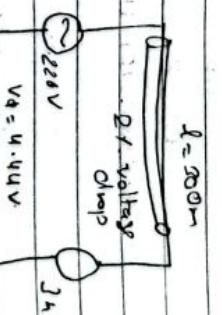


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

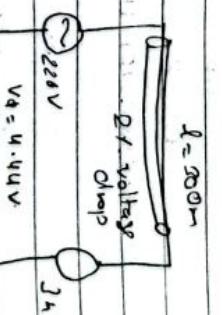


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

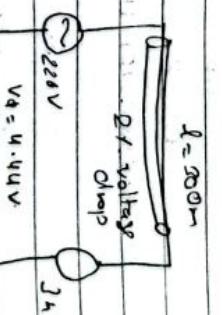


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

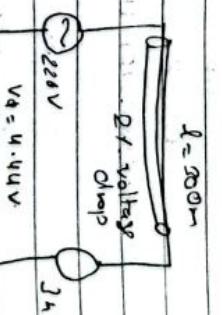


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

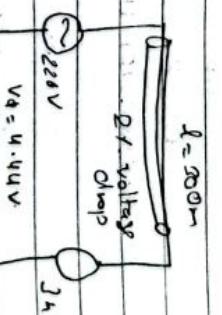


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

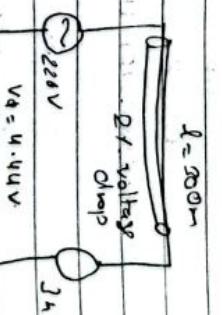


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

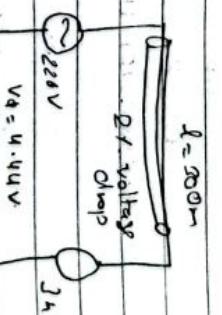


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

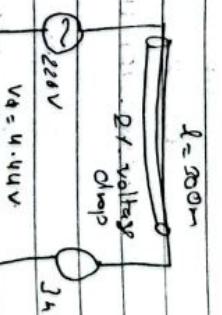


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

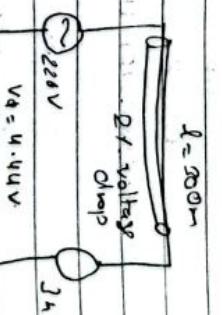


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

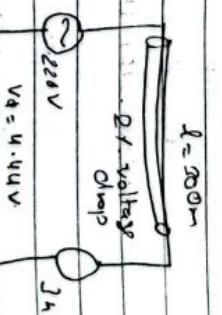


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

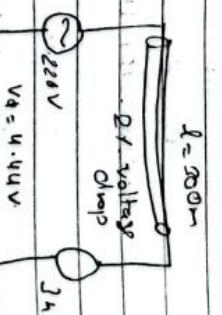


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

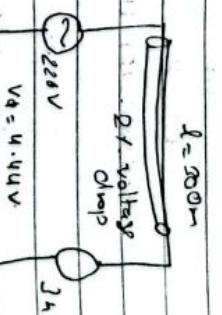


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

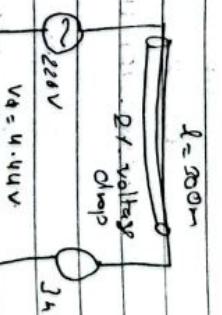


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

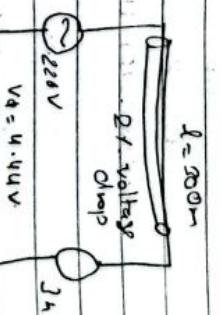


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

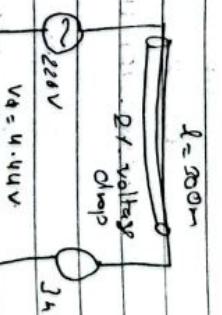


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

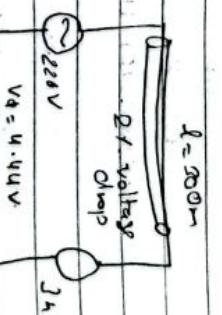


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

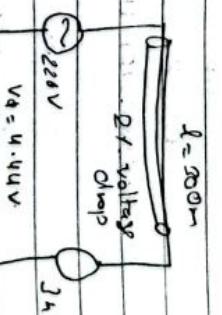


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

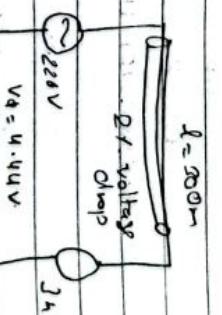


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

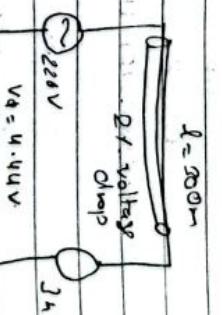


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

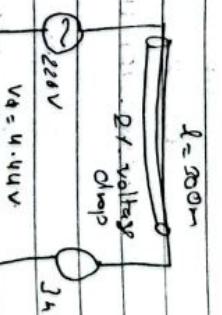


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

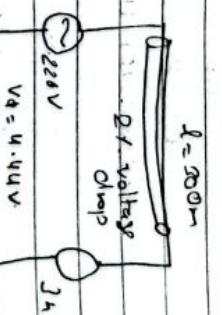


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

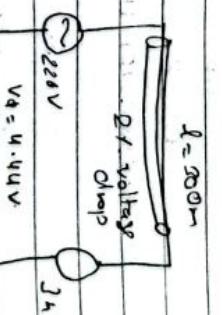


V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{1000} \times l$$

$$l = 22.9 \text{ mm}^2$$

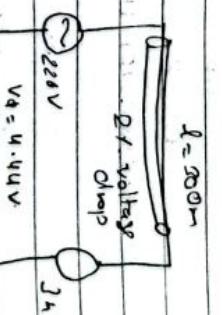

V_d

$$4.4 = 60 \times \frac{l}{R}$$

$$4.4 = \frac{4.238 \times 10^{-5} \text{ m}^2}{10$$

- Prevent at least minimize damage to equipment as a result of flow of heavy currents
- Improve the reliability of the power system

Classification of Earthing

- System earthing (connection between part of plant in operating system like LV neutral or a power transformer winding)
- Equipment Earthing (Safety grounding) connection of bodies of equipment (like electric motor body, transformer, Switchgear box, circuit breakers, etc) to earth.

Types of earthing:


a) Plate Type Earthing.

The earthing system, where copper or galvanized iron plate is used to connect all the earthing conductors to the earth is called plate type earthing. Generally, the plate is placed vertically at a depth not less than 3 meters or 10 feet from the ground level. Plate earthing is complex installation than rod earthing even it is most costly too.



12.5m
dia pipe

Earth
plate
90x90 Area

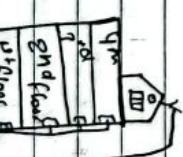

19mm dia
salt, coal sand
concrete
cement
copper
rod
earthing
plate
90x90 Area

b) Rod Type earthing / Pipe type earthing.

Pipe earthing is the process of using a metallic conductor to establish an electrical connection between two points in an electrical system. It's also known as "grounding" or "earth bonding". The most common type of pipe earthing metal pipes filled with concrete or other conductive materials that are buried in the ground. These pipes are then connected to a ground rod which is usually made of copper or another metal alloy.

Its advantages.
The main advantage of plate earthing is, it can carry a very high current than rod earthing. Also it provides a very good conductivity between earthing conduct and the ground.

It's disadvantage.


→ It has high installation cost.

→ It is more complicated than rod earthing.

2nd April



Classification
Page

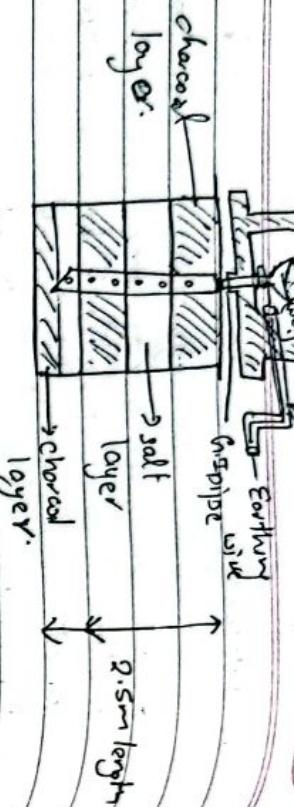

Electric shock and its Hazards:

Electric shock may be defined as dangerous event or conditions due to direct or indirect electrical contact with energized conductor or equipment and from which a person may sustain electrical injury from shock, damage to workplace environment, damage to property or both.

One can get shock by direct contact to the part of installation.

The effect of electrical current through the human body vary according to

- The voltage level.

- The time of current flow.

- The value of the current.

- Frequency of the network.

- Path of the current.

- The ability of the person to electrical installation with voltage up to 50V, in

- dry place and up to 25V in wet or humid place (AC) and up to 120V DC are considered safe in what concerns

- direct and indirect contact.

More dangerous DC of some level of voltage	AC (50Hz)	DC (mA)	Effects
0.5 - 1.5	0-4	Perception	
1-3	4-15	Surprise	
3 - 22	15-80	Reflex action	
22-40	80-160	Muscular contraction	
41-100	160-300	Respiratory block	
more than 100	300	Usually fatal	
more than 300			

Resistance of body depends on various factors like humid or wet skin weight, sex, age and the path of the human body it passes.

$$R = 100\Omega$$



The hazards of electrical shock are as follows.

- Loss of motion control → Burns

- Respiratory arrest → cardiac arrest

- Pain

- Physical fatigue.



- Burn

- cardiac arrest.


Chapter 3

Introduction to Electronics Engineering (14 M.W)

Electronics comprises the physics, engineering, technology and applications that deals with emission, flow and control of electronic & vacuum matter. This distinguished it from classical electrical engineering as it uses active devices to control electron flow by amplification rather than just passive effect such as resistance, capacitance and inductance.

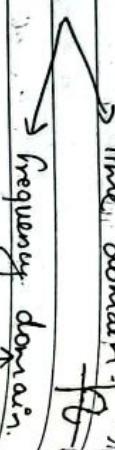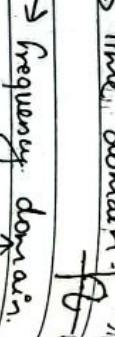Electrical Signals  

Signals are of different types i.e.

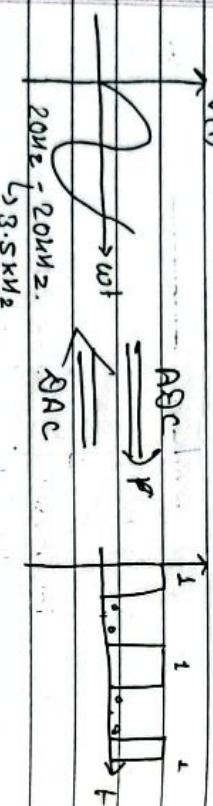

where, $T = \text{absolute temperature in K}$ at room temp of 300K

$$E_g = 0.735 - 2.23 \times 10^{-4} \times T \text{eV} \quad (\text{for Ge})$$

$$E_g \approx 1.1 \text{eV} \quad (\text{for Si})$$

$$E_g \approx 0.72 \text{eV} \quad (\text{for Ge})$$

Analog signal Digital signal.

At room temperature resistivity of semiconductor are in between insulator and conductors. Semiconductors show negative coefficient of resistivity i.e. resistance decreases with increase in temperature.

Semiconductor devices.

Both Si and Ge are elements of IV-group i.e. both elements have four valence electrons.

Semiconductor Devices

The materials that are neither conductor nor insulator with energy gap of about 1eV (electron Volt) are called semiconductors.

Most common materials commercially used as semi-conductors are given Germanium (Ge) and Silicon (Si) because their property to withstand high temperature. That means there will be no significant change in their energy gap with change in temperature.

$$E_g = 1.210 - 3.60 \times 10^{-4} \times T \text{eV} \quad (\text{for Si})$$

Both form the covalent bond with the neighbouring atom. At absolute zero temperature both behave like an insulator i.e. the valence bond is full while conduction band is empty but as the temperature is raised more and more covalent bonds break and electrons are set free and jump to the conduction band.

Intrinsic Semiconductor

As per theory of semiconductor, semi-conductors in its pure form is called as intrinsic semiconductor. In pure semiconductor number of electrons (n_i) is equal to number of holes (p) and thus conductivity is very low as valence electrons are co-valent bond.

In this case we can write $n = p = n_i$ where n_i is called intrinsic concentration. It can be shown as

$$n_i = n_0 T^{3/2} e^{-V_g/2kT}$$

where;

n_0 = constant

T = absolute temperature


V_g = Bond gap of semiconductor

V_t = Thermal voltage.

Extrinsic Semiconductors


As per theory of semiconductor, impure semiconductors are called extrinsic semiconductors. Extrinsic semiconductors is formed

N type

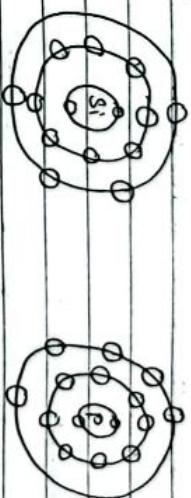

Doping
(-ve charge)


P-type

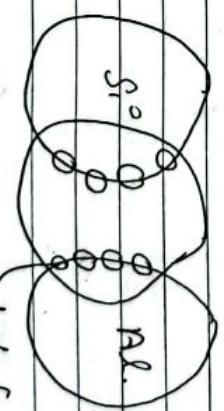


hole (P-type)

P-type

+ve charge.

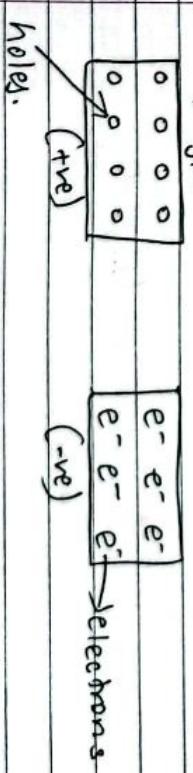

P-N junction

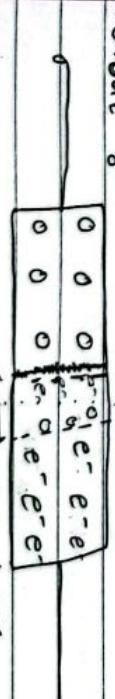


depletion layer.


by adding a small amount of impurity which is known as doping. Depending on the type of impurity we have two types of semiconductor i.e. N-type and P-type.

A diode is defined as a two terminal electronic components that only conducts current in one direction (So long as it operated within a specified voltage level).

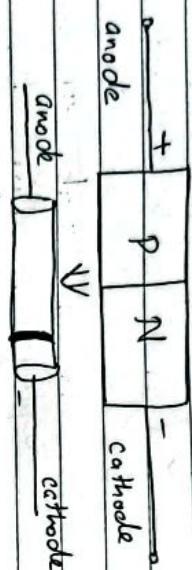An ideal diode will have zero resistance in one direction and infinite resistance in the reverse direction.



Symbol :-

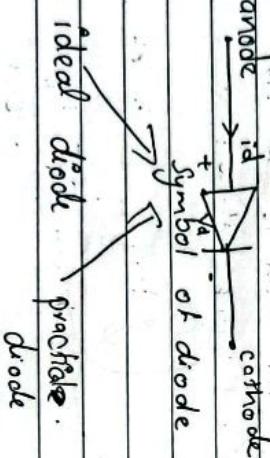

Its principle depends on the interactions of n-type and p-type semiconductors. In n-type semiconductor has plenty of free electrons and very few numbers of holes. In other word, we can say that the concentration of free electrons is high and that of holes in an n-type semiconductor. Free electrons in n-type semiconductor are referred as majority charge carrier, and holes in the n-type semiconductor are referred as minority charge carrier.

P-type	N-type
0	- + e ⁻ e ⁻
0	- + e ⁻ e ⁻ 0
0	- + e ⁻ e ⁻

depletion region.

i) Conduction.

$$i_d + V_a = id = \frac{V_a}{R_d} = \infty.$$

$$R_d = 0$$

ii) Reverse

$$id = 0$$

for practical diode

- i) Conduction $r_d = 0$ (min m)
 ii) Reverse $r_d \neq \infty$ (high)


6-April.

X Working principle of Diode.


The working principle of a diode depends on the interactions of n-type and p-type semiconductors. In n-type semiconductor has plenty of free electrons and very few numbers of holes. In other word, we can say that the concentration of free electrons is high and that of holes in an n-type semiconductor. Free electrons in n-type semiconductor are referred as majority charge carrier, and holes in the n-type semiconductor are referred as minority charge carrier.

Forward bias

Reverse Bias.

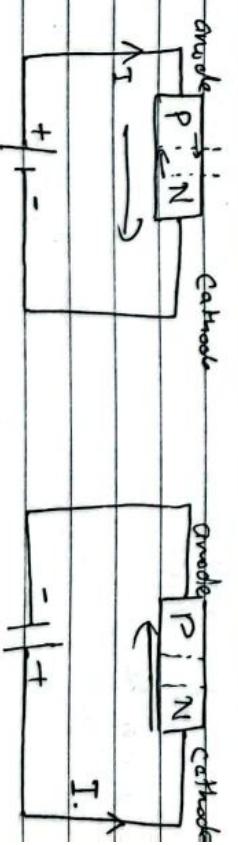

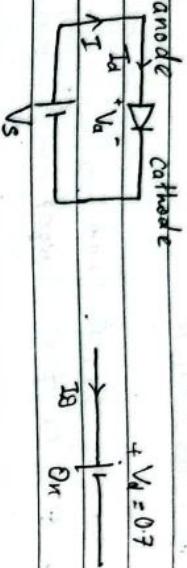f. anode \rightarrow cathode $+V_A = 0.7$




if $V_A > 0$ (forward bias) \rightarrow Ideal

if $V_A > 0.7V$ (Si) $\geq 0.3V$ (Ge) Non-ideal.

$$V_s = 0.7 + IR.$$


Eg : Reverse .

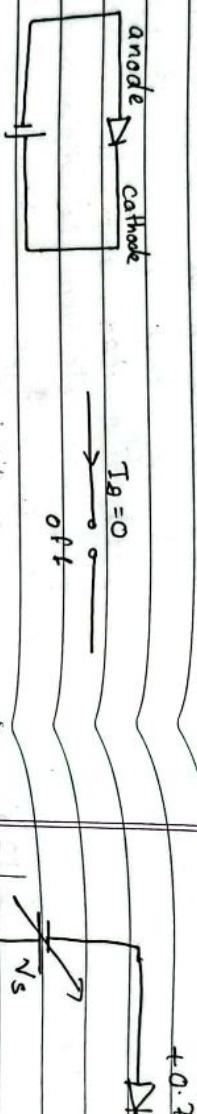

if $V_A < 0$ (Reverse bias) \rightarrow Ideal.

if $V_A < 0.7V \rightarrow$ practical.

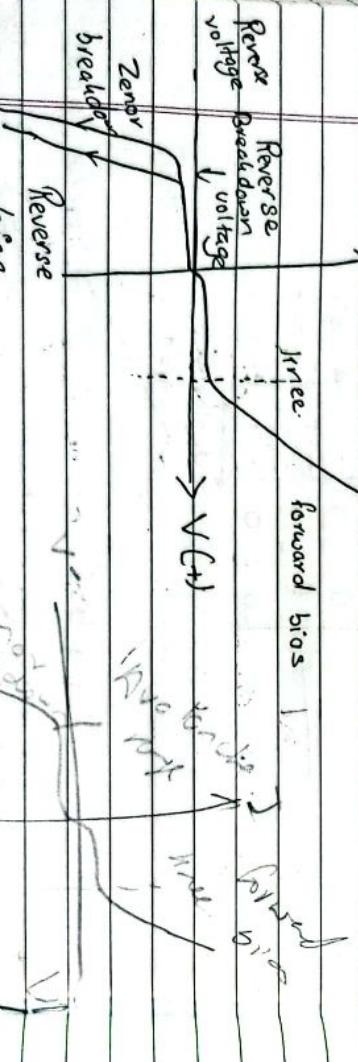Under reverse bias voltage junction barrier tends to increase with increase in bias voltage.




Zener diode is basically like an ordinary P-N junction diode but normally operates reverse biased conditions. But ordinary P-N junction diode connected in reverse biased condition is not used as Zener diode practically. A zener diode is a specially designed, highly doped P-N junction diode.

Avalanche Region.



Zener diode symbol.


Eg : Forward.

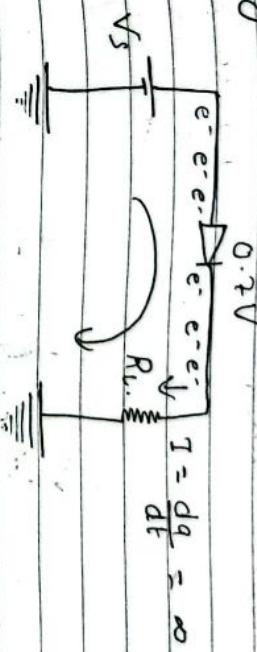

Eg: For the circuit shown below, find i) Output V


ii) Voltage drop across

series resistance.

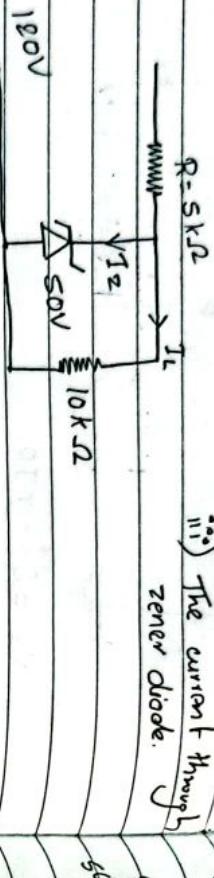


Ans: here,

Removing zener diode

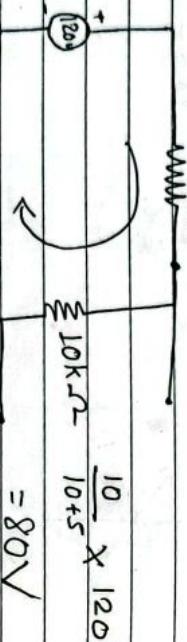

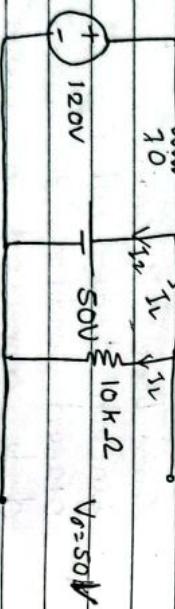Zener diode acts as voltage source because it is 'on state'. $R = 5\text{k}\Omega$




$$I = \frac{70}{5000} = 14\text{mA}$$





$$I_L = \frac{50}{10000} = 5\text{mA}$$

$$I_Z + I_L = I_L$$

Application of Diode.

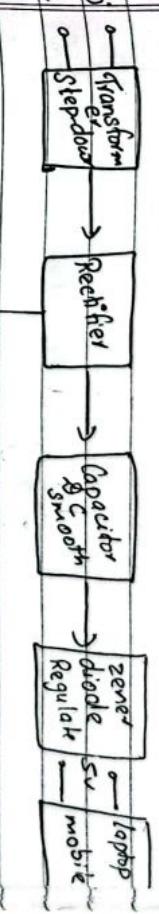
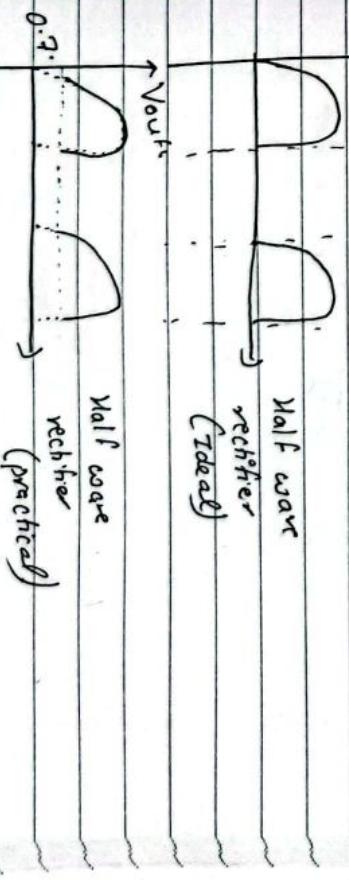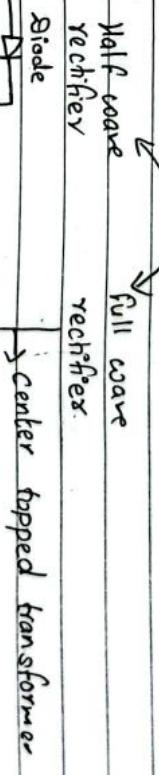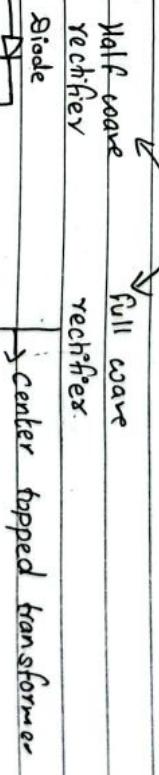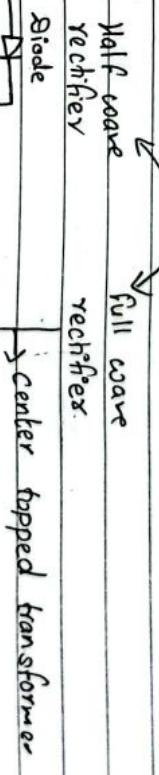
$$I_2 = I_L + I = -5 + 14 = +9\text{mA}$$



$$V(t) = V_m \sin(\omega t)$$

$$V_{avg} = \frac{1}{T} \int_0^T V(t) \cdot dt,$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T (V(t))^2 \cdot dt}$$

$$V_{avg} = \frac{1}{2\pi} \int_0^{2\pi} V_m \sin(\omega t) \cdot d(\omega t)$$

$$= \frac{V_m}{2\pi} \left[\int_0^{2\pi} \sin(\omega t) \cdot d(\omega t) \right]$$

$$= 2 \times \frac{V_m}{2\pi}$$

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (V_m \sin(\omega t))^2 \cdot d(\omega t)}$$


$$= \sqrt{\frac{V_m^2}{2\pi} \int_0^{2\pi} \sin^2(\omega t) \cdot d(\omega t)}$$

$$V_{rms} = \frac{V_m}{2}$$



rigid grid
Rectifier:

- a) half-wave Rectifier
- b) full-wave rectifier.

i) Center Tapped full-wave rectifier

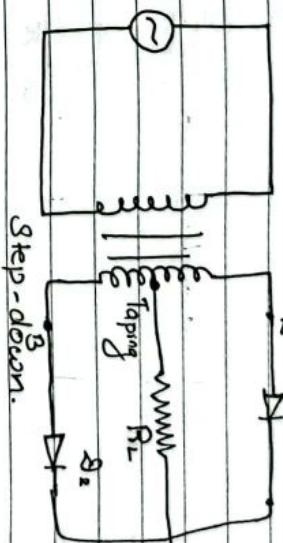

Step-down.

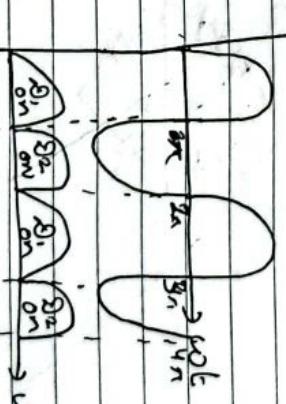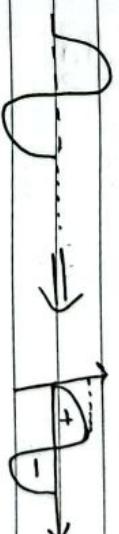

$$V_{avg} = \frac{1}{T} \int_0^T V(t) dt$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V^2(t) dt}$$

ii) Bridge Rectifier.

$$T = \pi$$



$$V(t) = V_m \sin(\omega t)$$

$$= \frac{1}{\pi} \int_0^\pi V_m \sin(\omega t) d(\omega t)$$

$$= \int_0^\pi \frac{1}{\pi} V_m \sin^2(\omega t) d\omega t$$

$$= \frac{V_m}{\pi} \left[\int_0^\pi \sin(\omega t) d(\omega t) \right] = \frac{V_m^2}{\pi} \cdot \frac{\pi}{2}$$

$$= \frac{V_m^2}{2}$$

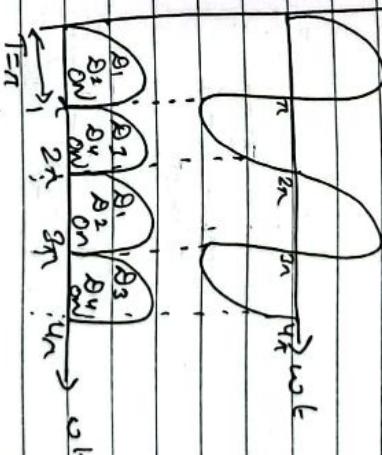
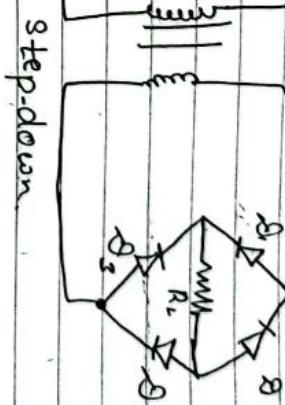


Capacitor

full wave and half wave

rectifier with a capacitor - input filter is used to

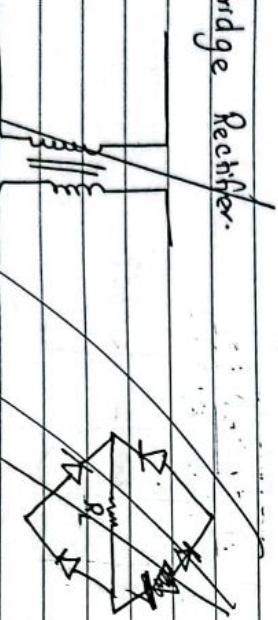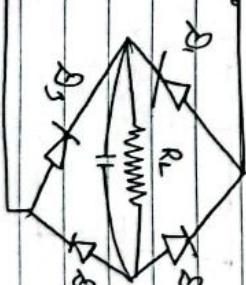smooth the wave form of output voltage. The value of capacitor depends on the level of output voltage.



ii) Half Wave Rectifier.

$$V(t) = V_m \sin(\omega t)$$


$$= \int_0^\pi V_m \sin^2(\omega t) d\omega t$$

$$= \frac{V_m^2}{\pi} \cdot \frac{\pi}{2}$$



$$= \frac{V_m^2}{2}$$

$$V_{avg} = \frac{1}{T} \int_0^T V(t) dt$$
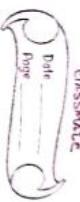
$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V^2(t) dt}$$


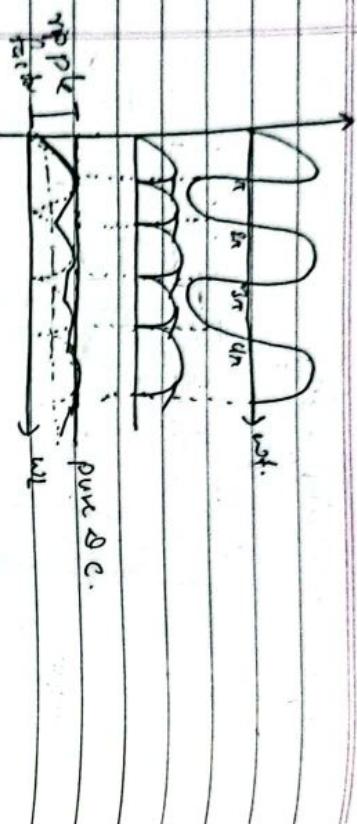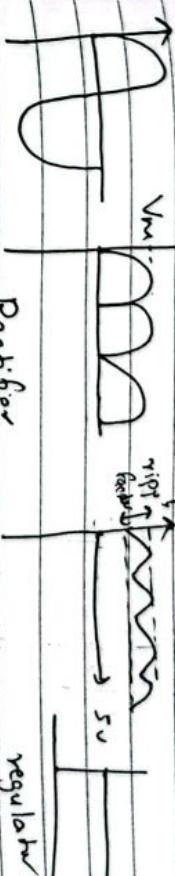
$$V_{avg} = 0 \quad V_{avg} = \frac{2V_m}{\pi}$$



$$\text{Ripple factor} = \sqrt{\left(\frac{V_{rms}}{V_{dc}}\right)^2 - 1} \quad r = \sqrt{\left(\frac{V_{rms}}{V_{dc}}\right)^2 - 1}$$

full wave

$$r = \sqrt{\left(\frac{V_{rms}}{V_{dc}}\right)^2 - 1}$$


= 1.21

$$\text{Ripple factor} = \sqrt{\left(\frac{V_{rms}}{V_{dc}}\right)^2 - 1}$$

$$= \sqrt{\left(\frac{\pi}{2}\right)^2 - 1}$$

$$= 0.48$$

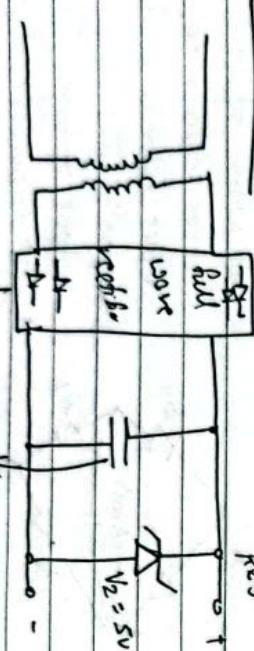Application of
Regulator (constant voltage)



smoothing form.
the wave

Continued....

Imp De-Morgan's Theorem.

There are two laws given by him that are as follows:-

$$\Rightarrow \text{1st law: } A+B = \bar{A} \cdot \bar{B}$$

Proof:


A	B	\bar{A}	\bar{B}	$A+B$	$\bar{A} \cdot \bar{B}$
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

$$\Rightarrow \text{2nd law: } \bar{A} \cdot \bar{B} = \bar{A} + \bar{B}$$


Proof:

A	B	\bar{A}	\bar{B}	$\bar{A} \cdot \bar{B}$	$\bar{A} + \bar{B}$
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
0	0	0	0	0	0

NAND Gate:

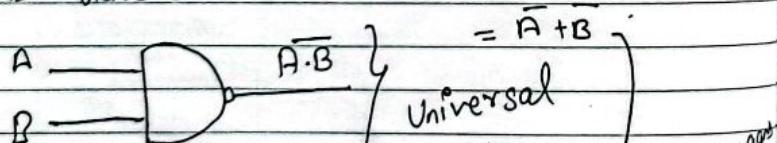


NOR Gate:

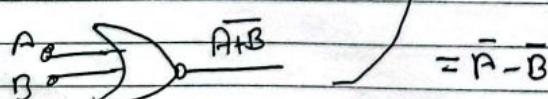


De-Morgan's Theorem




XOR

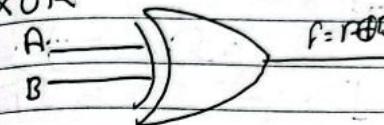

Why NAND Gate and NOR Gate are called universal gate?

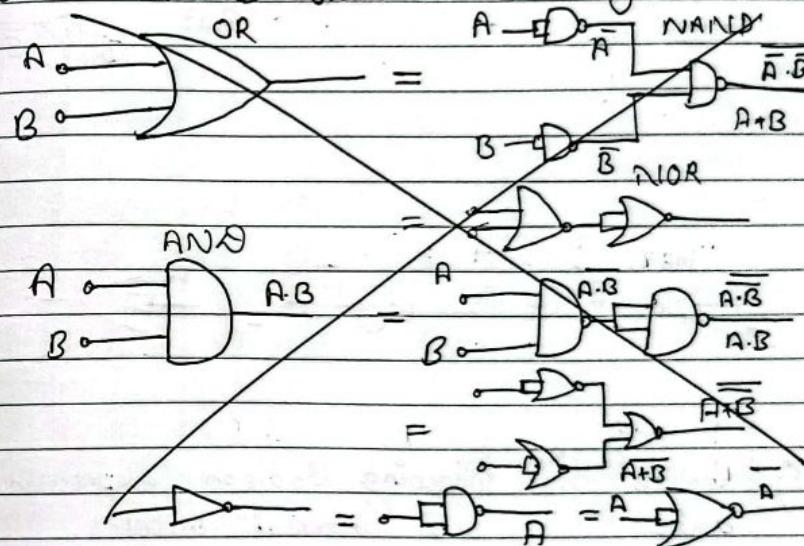
→ Because all the other gate can be replaced with NAND Gate or NOR gate i.e



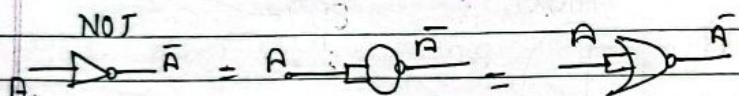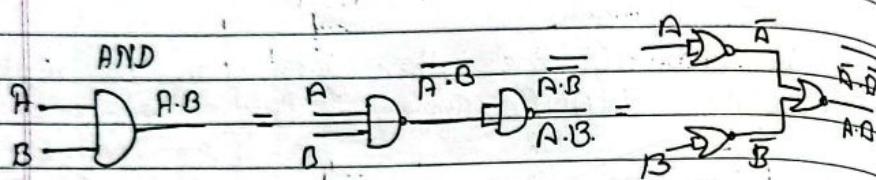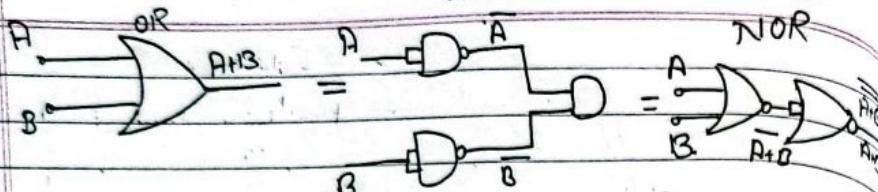

Eg. Realize the following Boolean expression using basic gates and universal gates.

$$Y = (A \cdot B) + (B \cdot C)$$

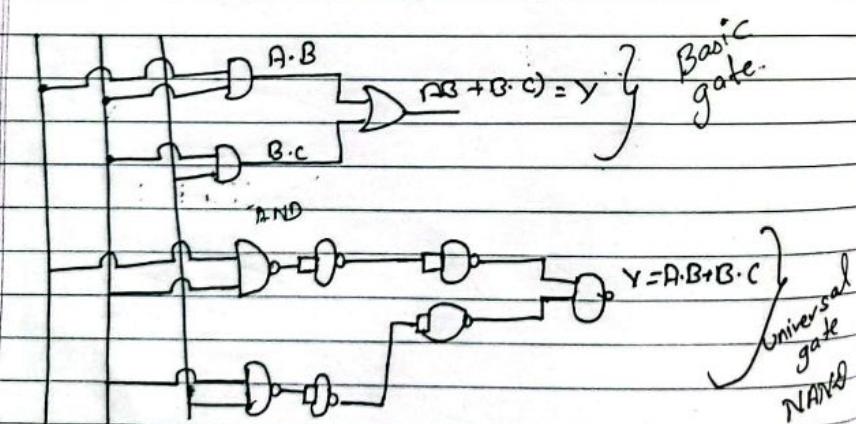

Representation of Boolean Expression:

The relationship between boolean expression variables and output variable is called Boolean expression. the Boolean expression can be represented in two different forms, they are;

- i) Sum of products (SOP) form
- ii) Product of sums (POS) form.

Eg :

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

$f = \text{SOP}$

SOP,


$$Y = \overline{A} \cdot \overline{B} \cdot C + \overline{A} \cdot B \cdot \overline{C} + A \cdot \overline{B} \cdot \overline{C} + A \cdot \overline{B} \cdot C + A \cdot B \cdot C$$

POS:

~~$$Y = \overline{A} \cdot \overline{B} \cdot \overline{C} + A \cdot B \cdot C$$~~

POS
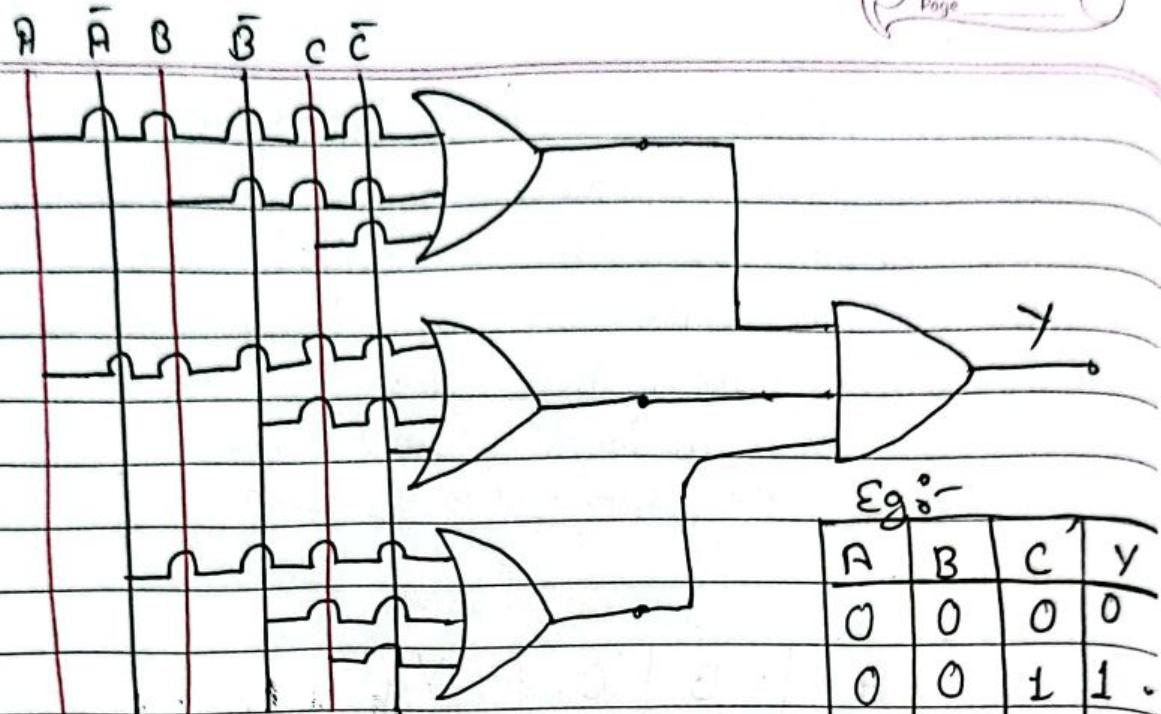
$$Y = (A + B + C) \cdot (A + \overline{B} + \overline{C}) \cdot (\overline{A} + \overline{B} + C)$$



Eg:-

A	B	C	y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

SOP

$$y = \bar{A} \cdot \bar{B} \cdot C + \bar{A} \cdot B \cdot \bar{C} + A \cdot \bar{B} \cdot C + A \cdot B \cdot C + ABC$$

POS

$$y = (A+B+C) \cdot (A+\bar{B}+\bar{C}) \cdot (\bar{A}+B+C)$$

